

# **Chapter 4**

## **The Processor**

**Computer Architecture and Organization**  
**School of CSEE**

# 1. Review

- Logic design review
- MIPS instruction review

## 2. Building Datapath

## 3. A Simple Implementation Scheme

A close-up image of a microchip with a square gold pad in the center and numerous pins around the perimeter.

# Introduction

- **In this section, we will review several issues covered in Logic Design course.**
- **Make sure that you know the difference between combinational circuit and sequential circuit.**
- **Also be aware of the behavior of synchronous sequential circuit.**




# Two Types of Implementation Components


- Elements that **operate on data** values (combinational) : e.g. ALU
  - combinational : outputs depends only on the current inputs (same input → same output)
- Elements that **contain state** (sequential) : e.g. memory and registers
  - sequential : outputs depends on the current inputs and current state. (same input → possibly different output)

# Review : Combinational Logic Elements


- Adder

 

- MUX

 

- ALU

 

AND



NAND



OR



NOR




XOR



NOT


 
# Review : State Elements

- **Unclocked vs. Clocked (Asynchronous vs. Synchronous)**
- **Clocks used in synchronous logic – edge triggered (vs. master-slave)**
  - when should an element that contains state be updated?



 
 
# Review : D-latch

- **Two inputs:**
  - the data value to be stored (D)
  - the clock signal (C) indicating when to read & store D
- **Two outputs:**
  - the value of the internal state (Q) and it's complement
- **The output is complemented while clock signal is active.**


 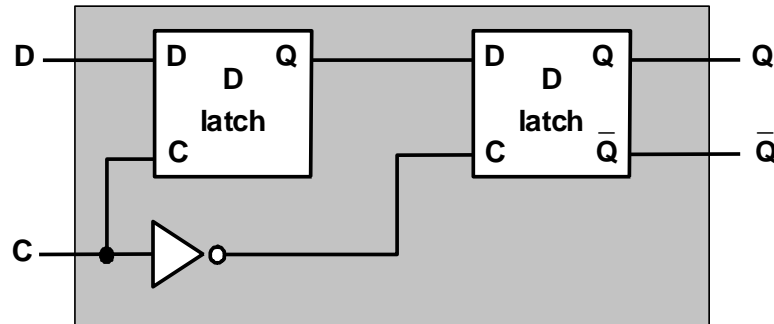
# Review : D flip-flop


- Output changes only on the clock edge
- Master-Slave flip-flop : have ones (or zeros) catching problem






# Review : D flip-flop

- Edge-triggered flip-flop

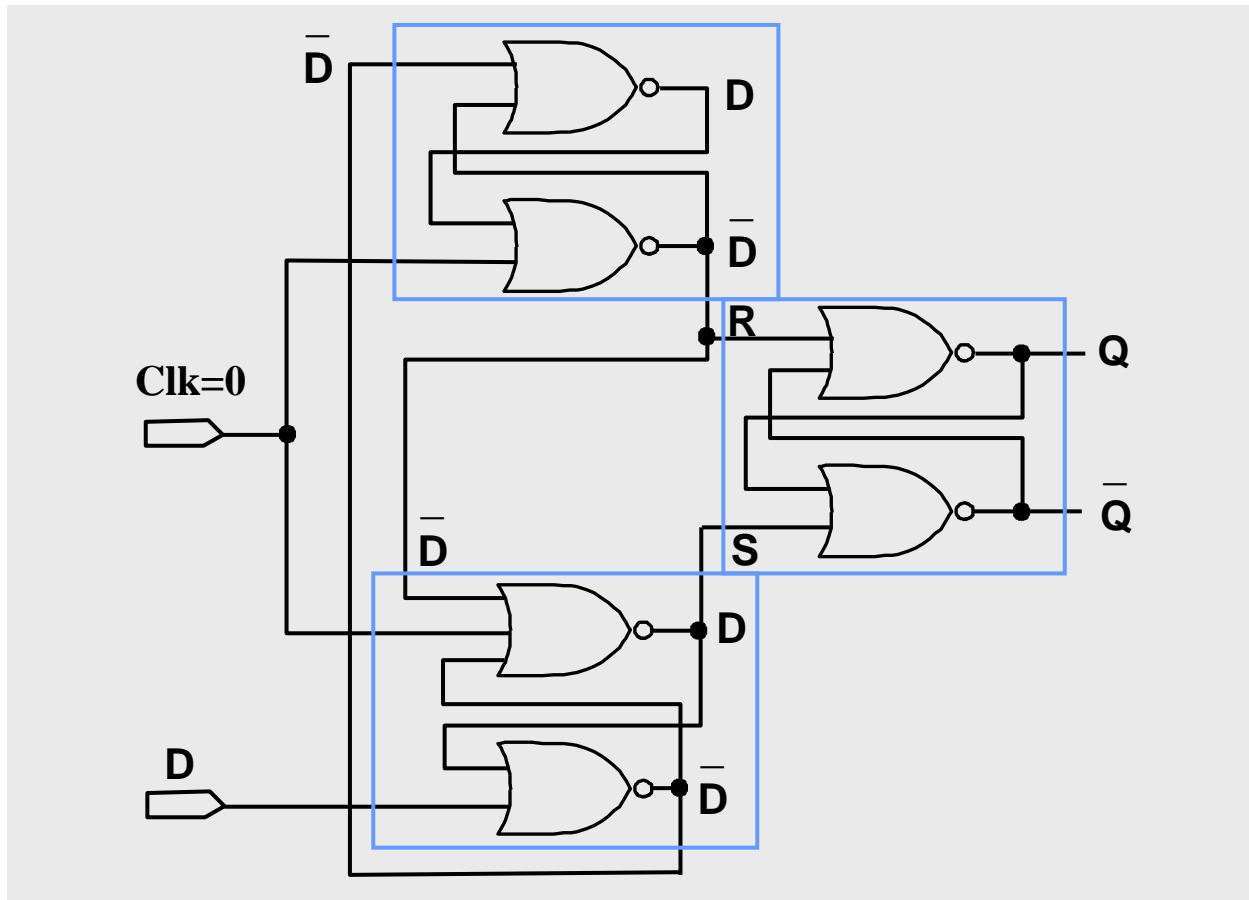
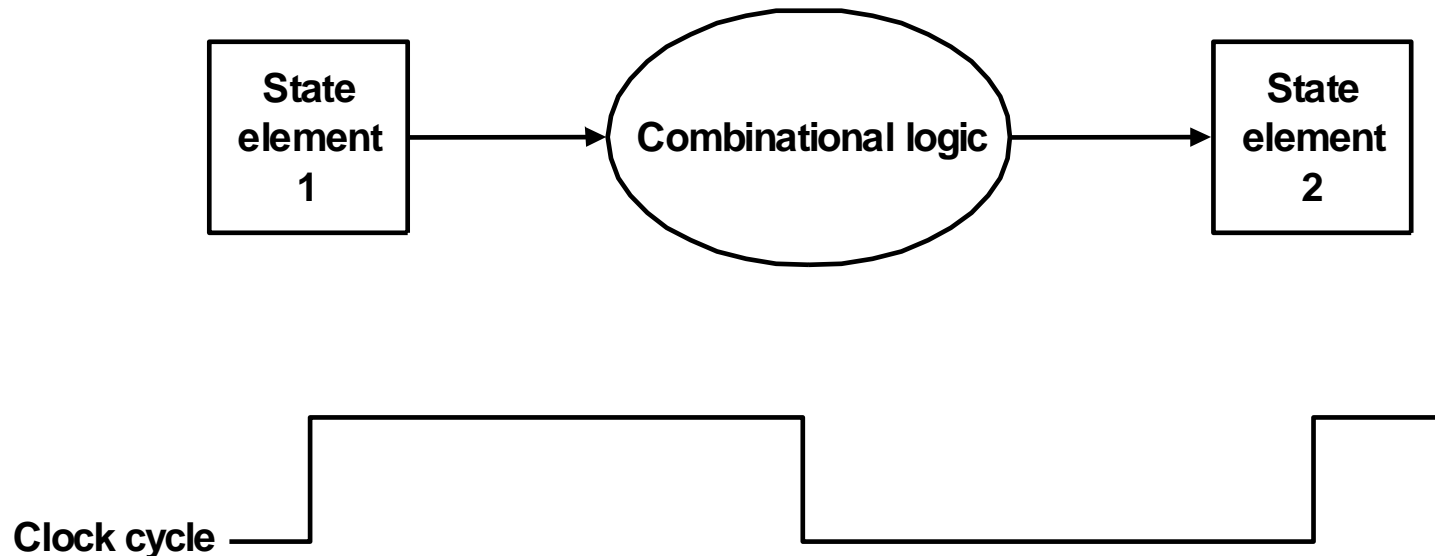
# Review : Our Implementation

- An edge triggered methodology
- Typical execution:
  - read contents of some state elements,
  - send values through some combinational logic
  - write results to one or more state elements





# Exercise


**Explain the difference between synchronous sequential circuit and asynchronous sequential circuit.**

# Summary

- In sequential circuit the output depends on present state and input, while the output depends only on input in combinational circuit.
- In synchronous sequential circuit there is a special signal called 'clock' which synchronize the action of all components.

# Instruction format Summary

- Three MIPS Instruction Formats:

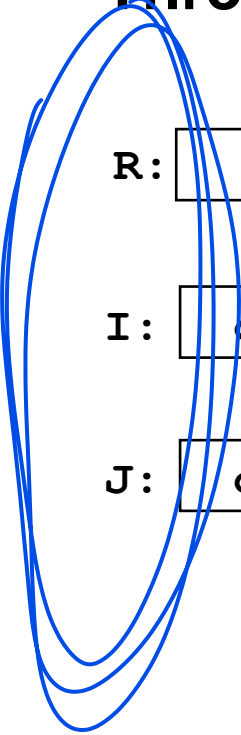

R:	op	rs	rt	rd	shamt	funct
----	----	----	----	----	-------	-------

I:	op	rs	rt	constant or address
----	----	----	----	---------------------

J:	op	jump address (word address)
----	----	-----------------------------

# Instruction Summary

Category	Format	Instruction	Format	Meaning
Arithmetic	R	ADD	ADD rd,rs,rt	$rd \leftarrow rs + rt$
	R	SUB	SUB rd,rs,rt	$rd \leftarrow rs - rt$
	I	ADDI	ADDI rt,rs,imm16	$rt \leftarrow rs + se(imm16)$
	R	SLT	SLT rd,rs,rt	$rd \leftarrow (rs < rt) ? 1 : 0$
	I	SLTI	SLTI rt,rs, imm16	$rt \leftarrow (rs > se(imm16)) ? 1 : 0$
Logical	R	AND	AND rd,rs,rt	
	R	OR	OR rd,rs,rt	
	I	ANDI	ANDI rt,rs,imm16	$rt \leftarrow rs \& ze(imm16)$
	R	NOR	NOR rd, rs, rt	
	R	SLL	SLL rd, rs, shamt	
	R	SRL	SRL rd, rs, shamt	
Data Transfer	I	LW	LW rt, imm16(rs)	$rt \leftarrow M[rs+se(imm16)]$
	I	SW	SW rt, imm16(rs)	$M[rs+se(imm16)] \leftarrow rt$
Control Transfer	I	BEQ	BEQ rs,rt, imm16	if (rs == rt) $PC \leftarrow PC+se(imm16)*4$
	I	BNE	BNE rs,rt, imm16	If (rs != rt) $PC \leftarrow PC+se(imm16)*4$
	R	JR	JR rs	$PC \leftarrow rs$
	J	JAL	JAL imm26	$\$ra \leftarrow PC+4; PC \leftarrow imm26*4$
	J	J	J imm26	$PC \leftarrow imm26*4$

## 1. Review

- Logic design review
- MIPS instruction review

## 2. Building Datapath

## 3. A Simple Implementation Scheme

- In this section we will learn basic datapath for single clock cycle datapath. The instruction is executed in one clock cycle in single clock cycle CPU.
- The datapath is arranged according to the MIPS instruction set.



# The Processor: Datapath & Control


- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
  - memory-reference instructions: `lw`, `sw`
  - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
  - control flow instructions: `beq`, `j`
- Generic Implementation:

- fetch*
1. use the program counter (PC) to supply **instruction address**
  2. get the instruction from memory
- execution*
3. read registers
  4. use the instruction to **decide exactly what to do**

→ Stored Program Concept



# add Operation

 

● add                  rd, rs, rt

IR ← mem[PC];  
R[rd] ← R[rs] + R[rt];  
PC ← PC + 4;

## RTL Description

Fetch instruction from memory

ADD operation


Calculate next address

Register Transfer Language

RTL



# sub Operation

 

● add          rd, rs, rt

$IR \leftarrow \text{mem}[PC];$

$R[rd] \leftarrow R[rs] + \sim R[rt] + 1;$

$PC \leftarrow PC + 4;$

2's compl-

## RTL Description


Fetch instruction from memory

SUB operation

Calculate next address



# lw Operation

 


## ● lw                      rt, rs, imm16

```
IR ← mem[PC];  
Addr ← R[rs] + SignExt(imm16);  
R[rt] ← Mem[Addr];  
PC ← PC + 4;
```

 
## RTL Description

Fetch instruction from memory  
Compute memory address  
Load data into register  
Calculate next address





# sw Operation

 


## ● sw rt, rs, imm16

```
IR ← mem[PC];  
Addr ← R[rs] + SignExt(imm16);  
Mem[Addr] ← R[rt];  
PC ← PC + 4;
```

 
## RTL Description

Fetch instruction from memory  
Compute memory address  
Store data into memory  
Calculate next address





# beq Operation

 

## ● beq      rt, rs, imm16

$IR \leftarrow \text{mem}[PC];$

$\text{Cond} \leftarrow R[\text{rs}] + \sim R[\text{rt}] + 1;$

$PC \leftarrow \text{Cond} ? PC + 4;$

          :  $PC + 4 + (\text{SignExt}(\text{imm16}) \ll 2)$

## RTL Description

Fetch instruction from memory


Compute conditional Cond

Fall through if non-zero Cond

Branch if zero Cond

**However, the instruction won't be stored in IR in single clock cycle implementation. Why?**

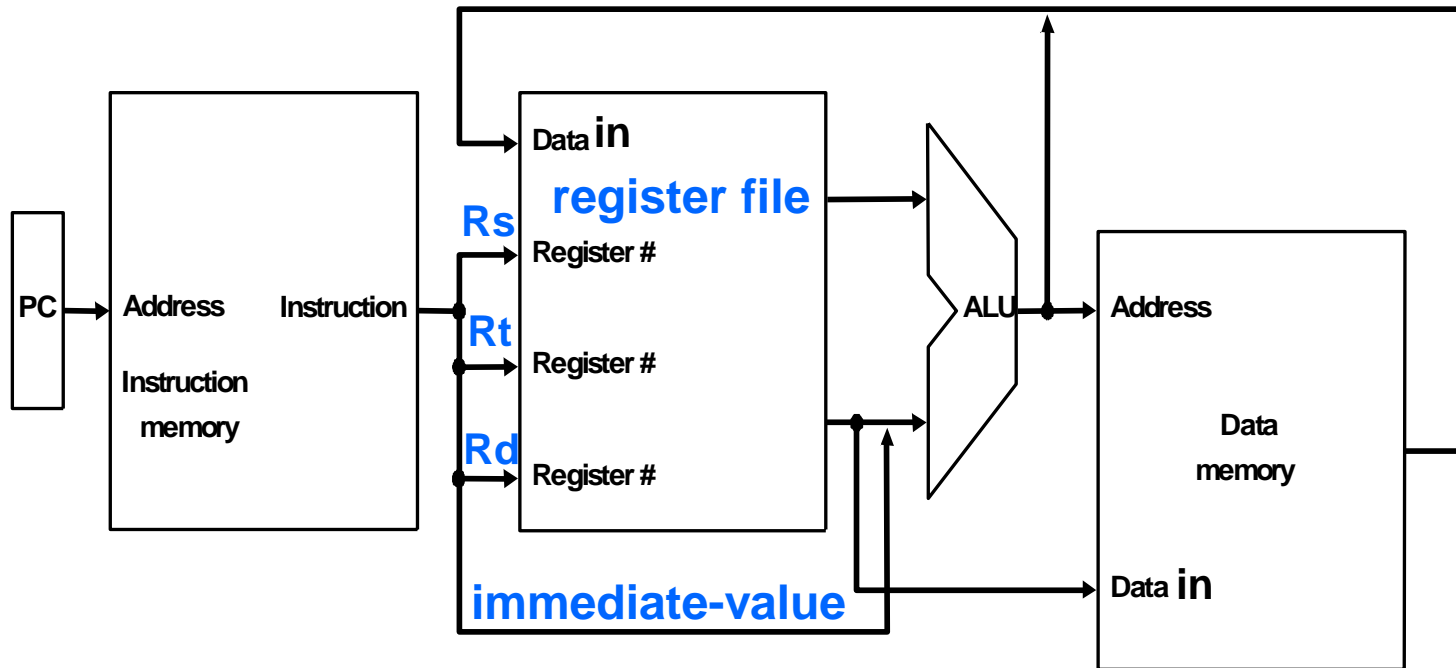
# Abstract/Simplified View of Implementation



**We need separate memory for instruction and data.  
Why?**

# Register File


- Has been built using D flip-flops

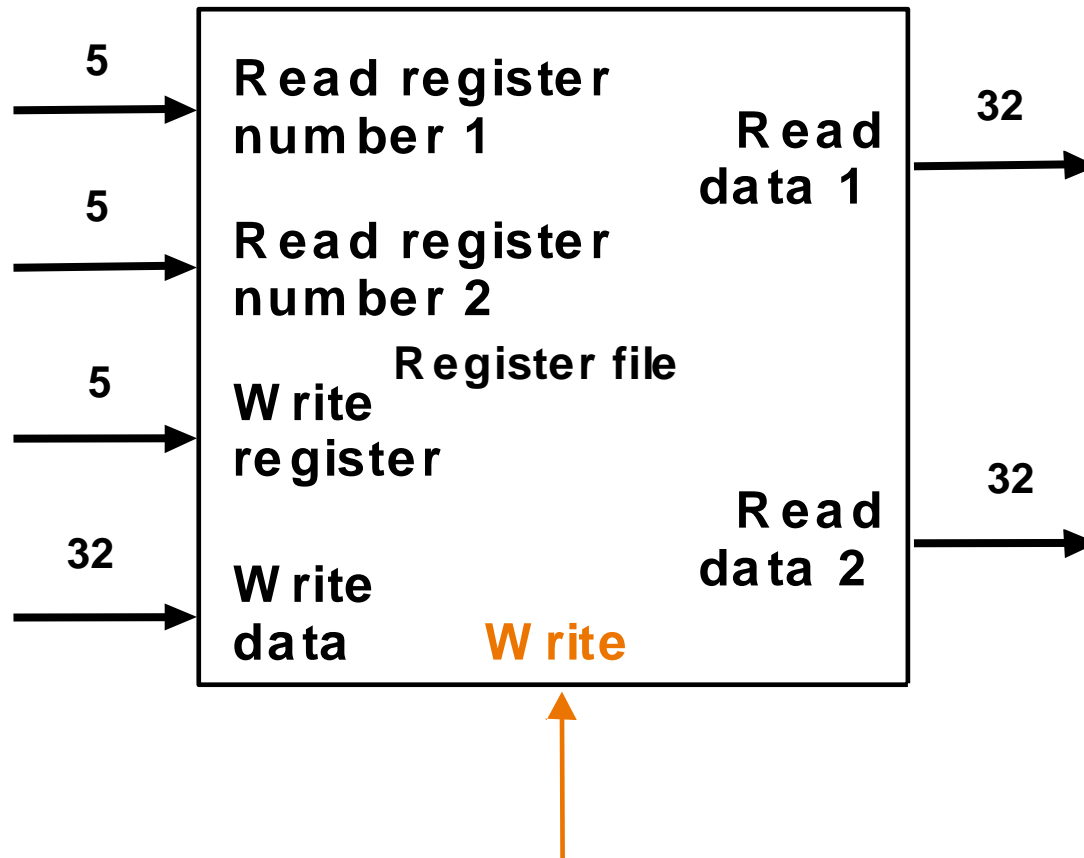




# Register File

- Has been built using D flip-flops

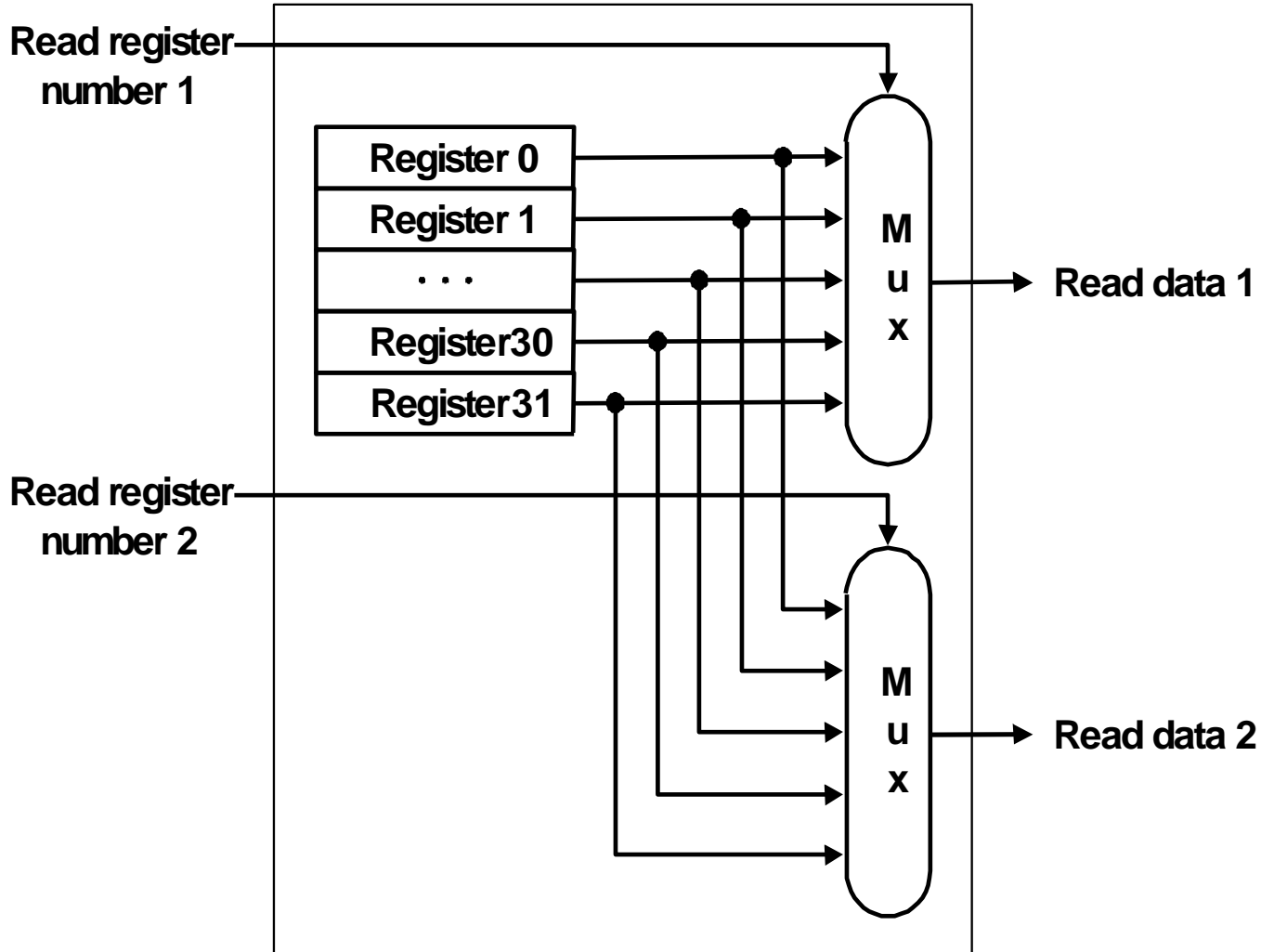

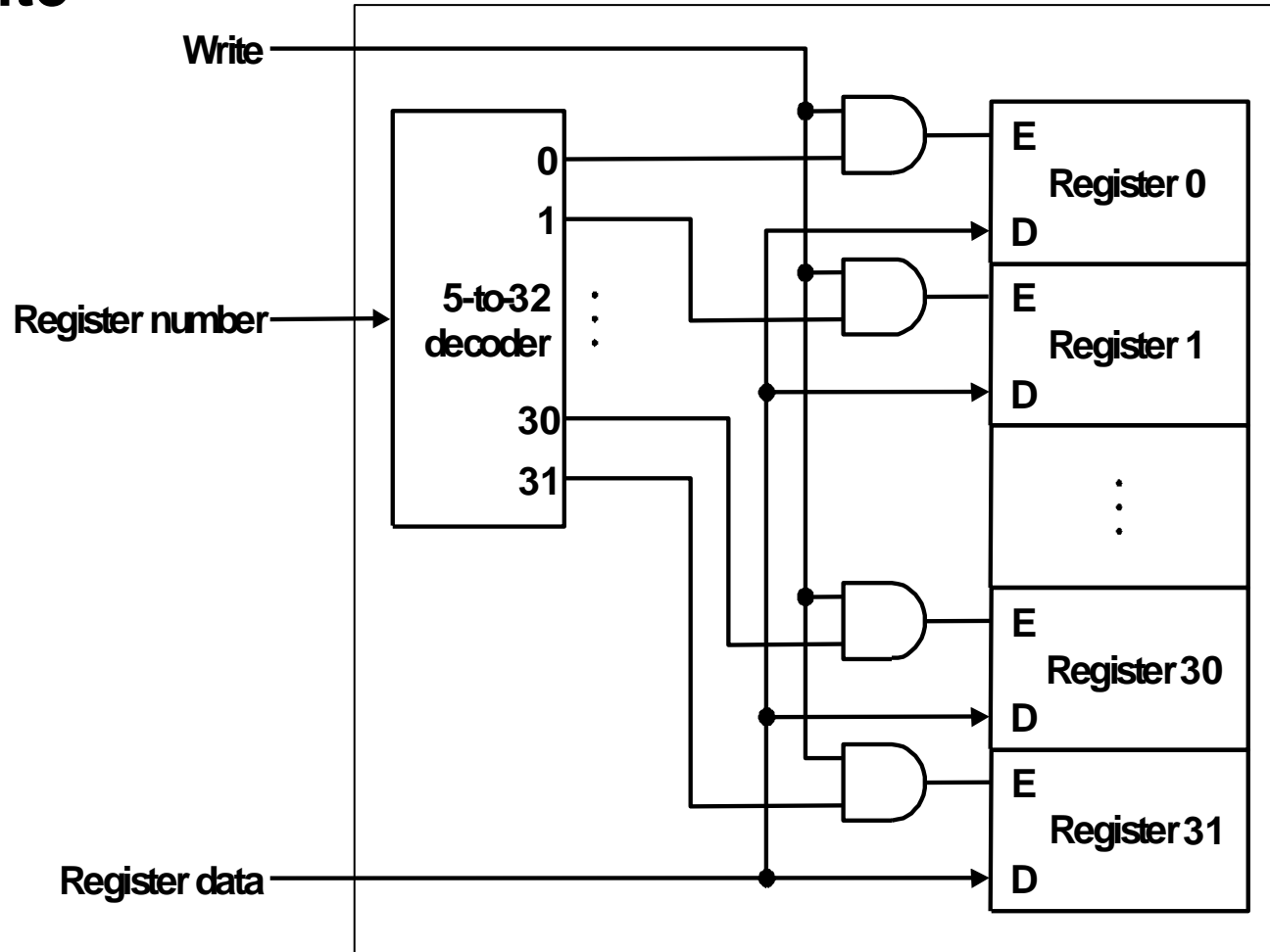
# Register File

- Note: we still use the real clock to determine when to write**



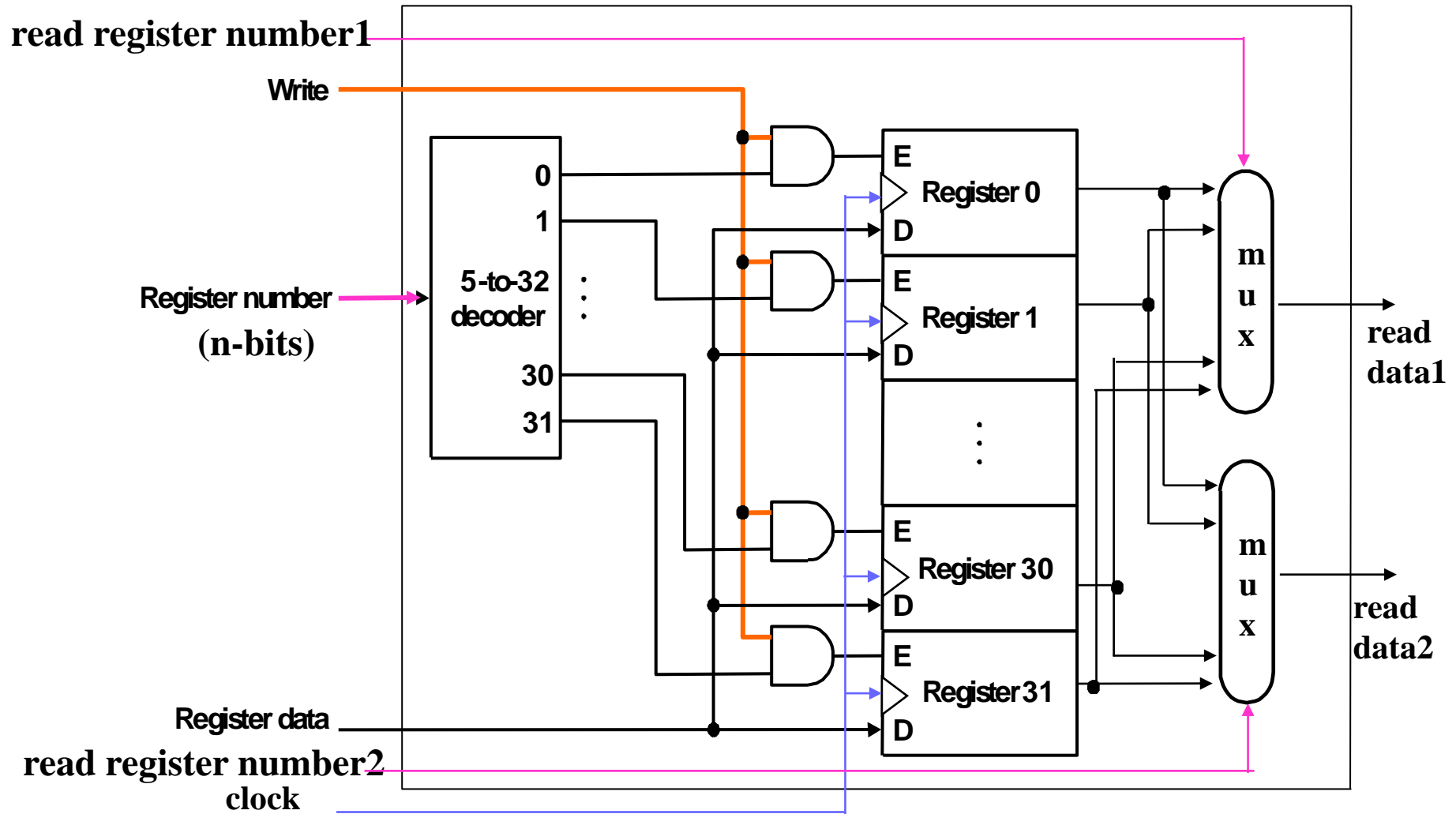
# Register File

- Note: We can read and write at the same time!**


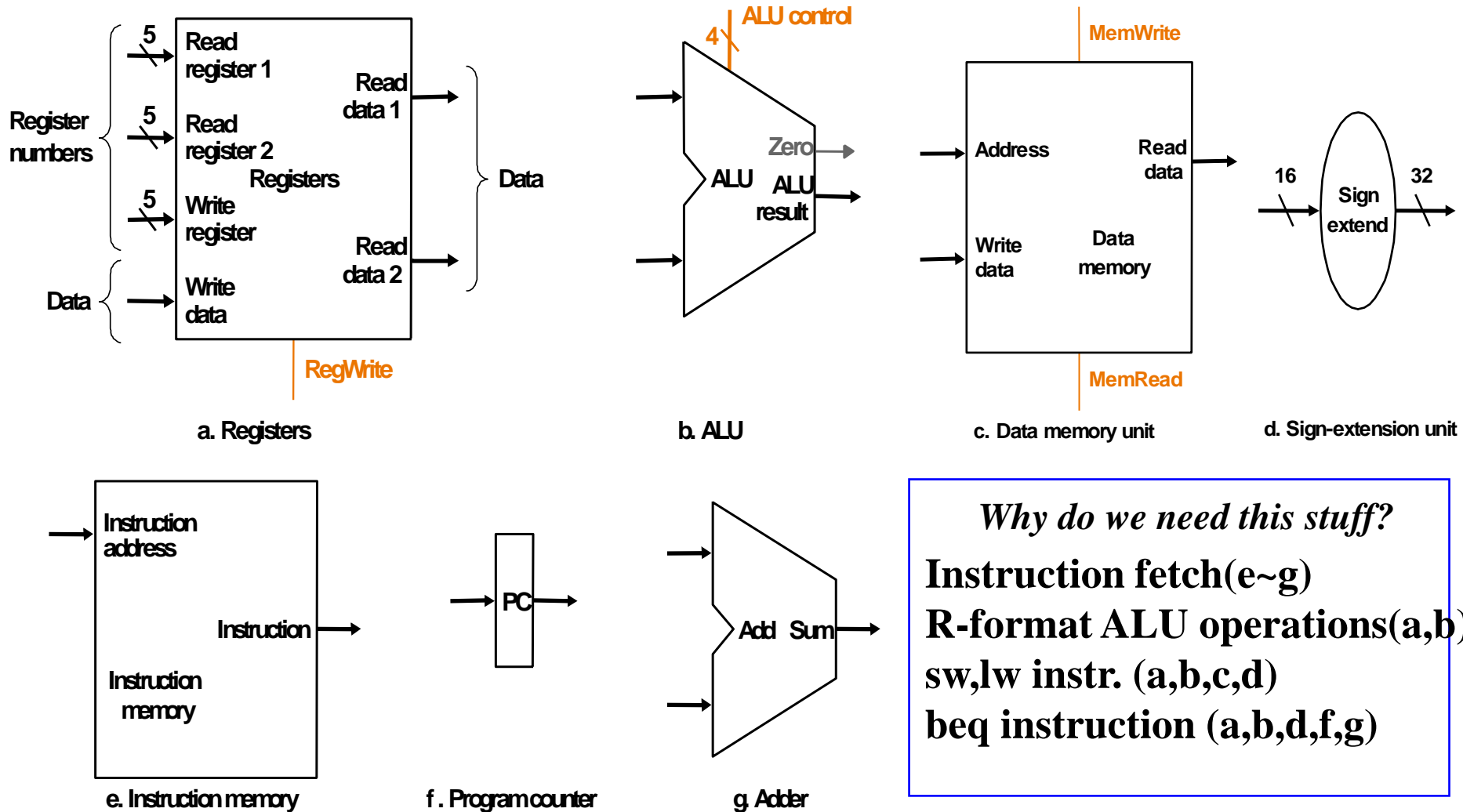
# Components for Simple Implementation


- Include the functional units we need for each instruction



*Why do we need this stuff?*

**Instruction fetch(e~g)**  
**R-format ALU operations(a,b)**  
**sw,lw instr. (a,b,c,d)**  
**beq instruction (a,b,d,f,g)**


# ALU with 4 control signals

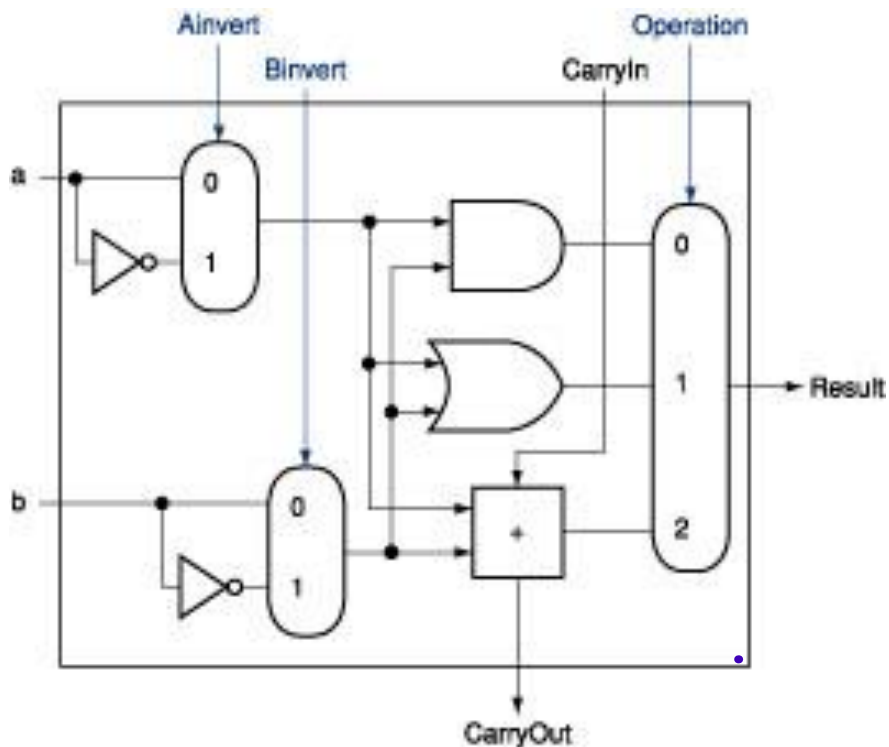

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR



# MIPS ALU

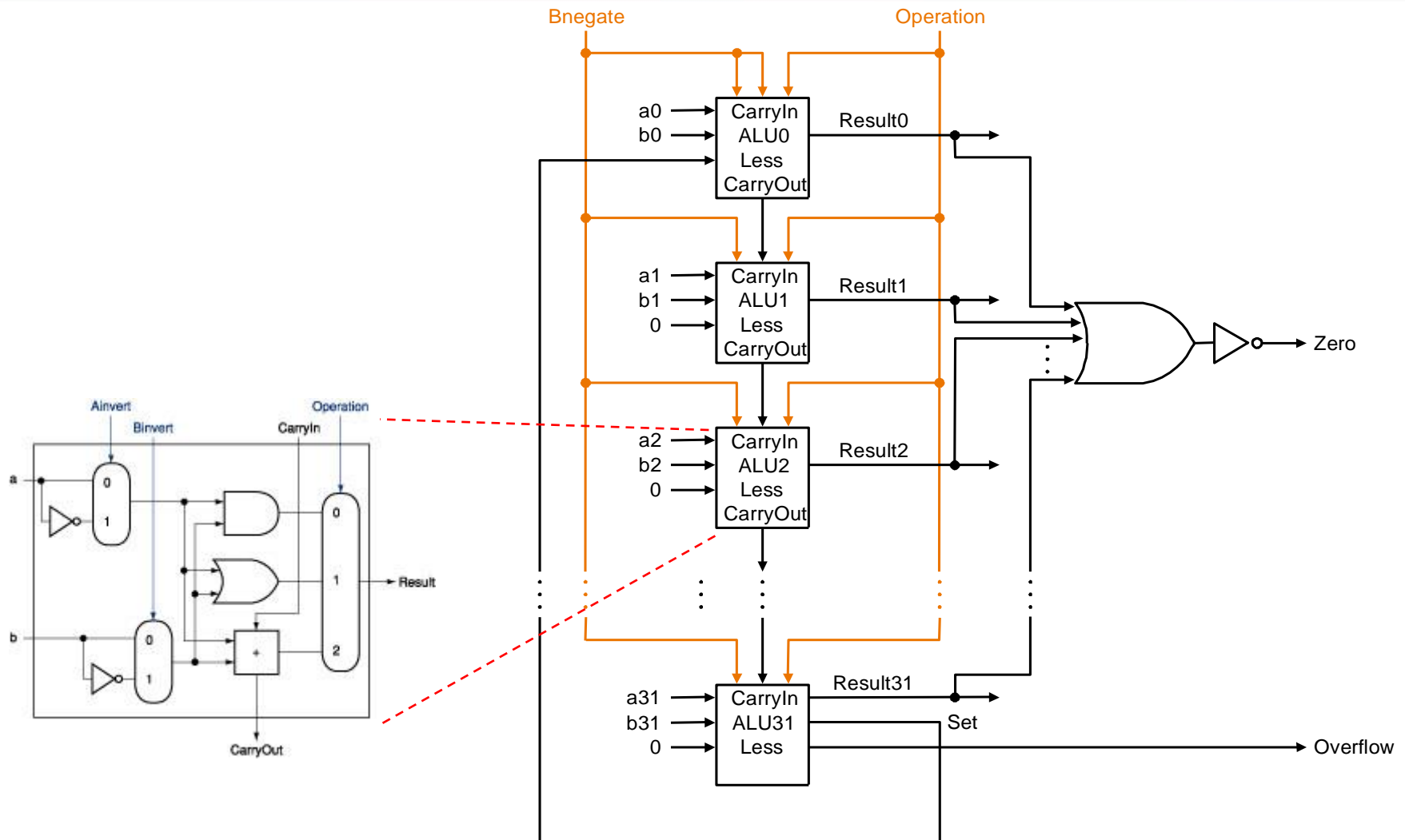


•Note: zero is 1 when the result is zero!

## Status bits (or condition code)


1. **Z : zero** –  $\begin{cases} 1 & \text{if result is 0} \\ 0 & \text{if result is non-zero} \end{cases}$
2. **S : sign** –  $\begin{cases} 0 & \text{if result is positive number} \\ 1 & \text{if result is negative number} \end{cases}$
3. **V : overflow** –  $\begin{cases} 0 & \text{if overflow does not occur} \\ 1 & \text{if overflow occurs} \end{cases}$
4. **C : carryout** –  $\begin{cases} 0 & \text{if there is a carryout} \\ 1 & \text{if there is no carryout} \end{cases}$

# Instruction Fetch Datapath

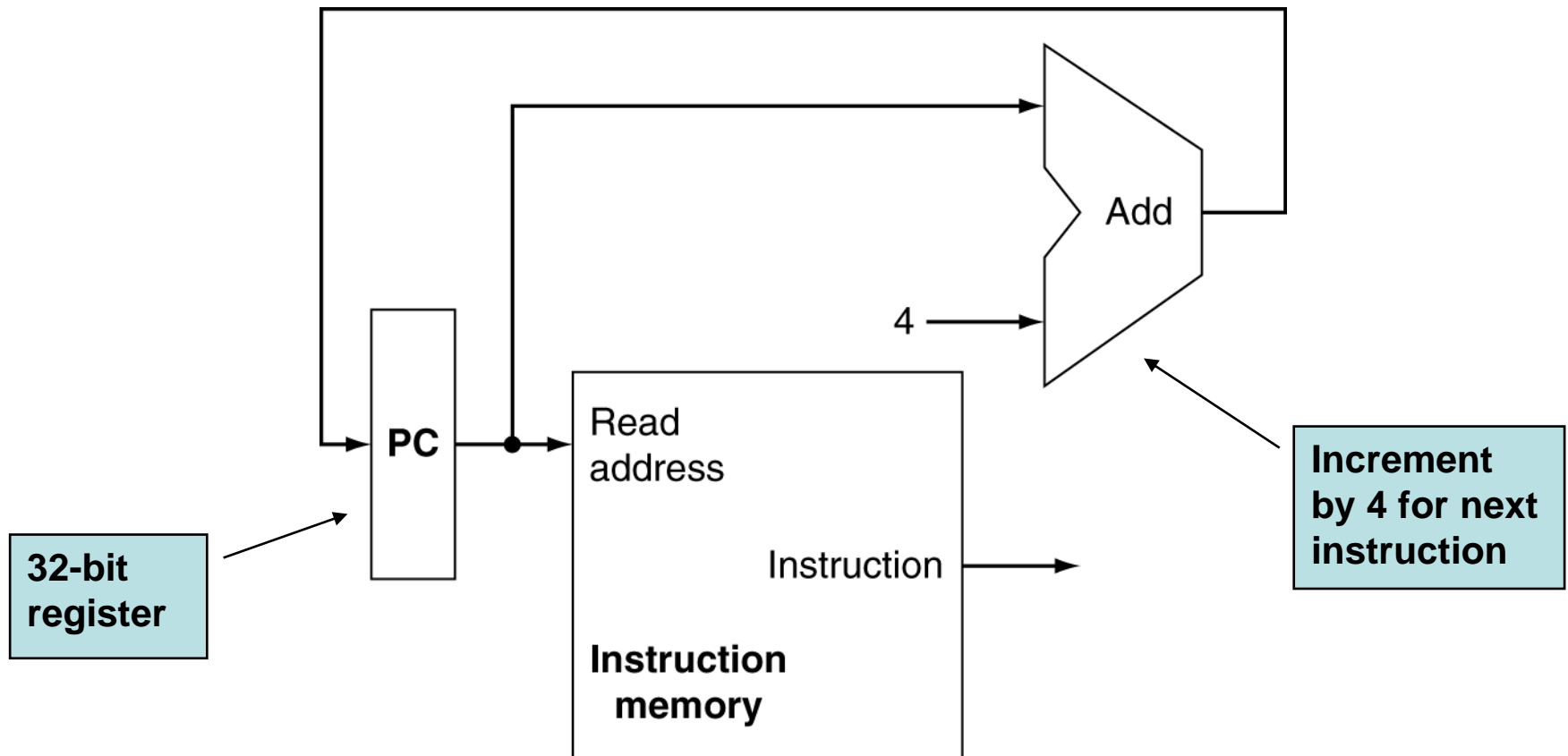




# Datapath for R-type Instructions

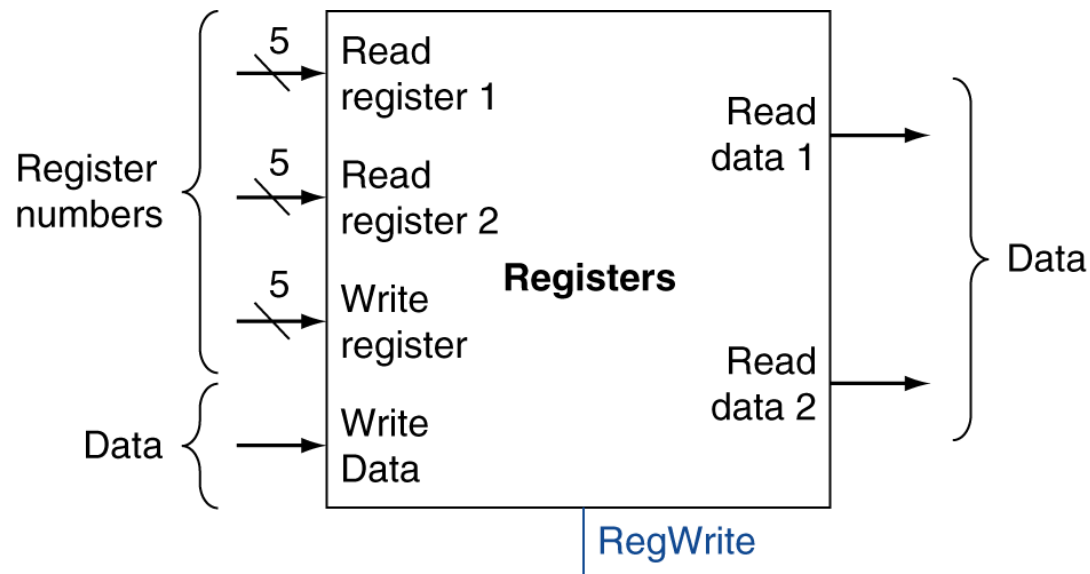


a. Registers

 


b. ALU

**add, sub, and, or, slt**

# Datapath for a Load or Store

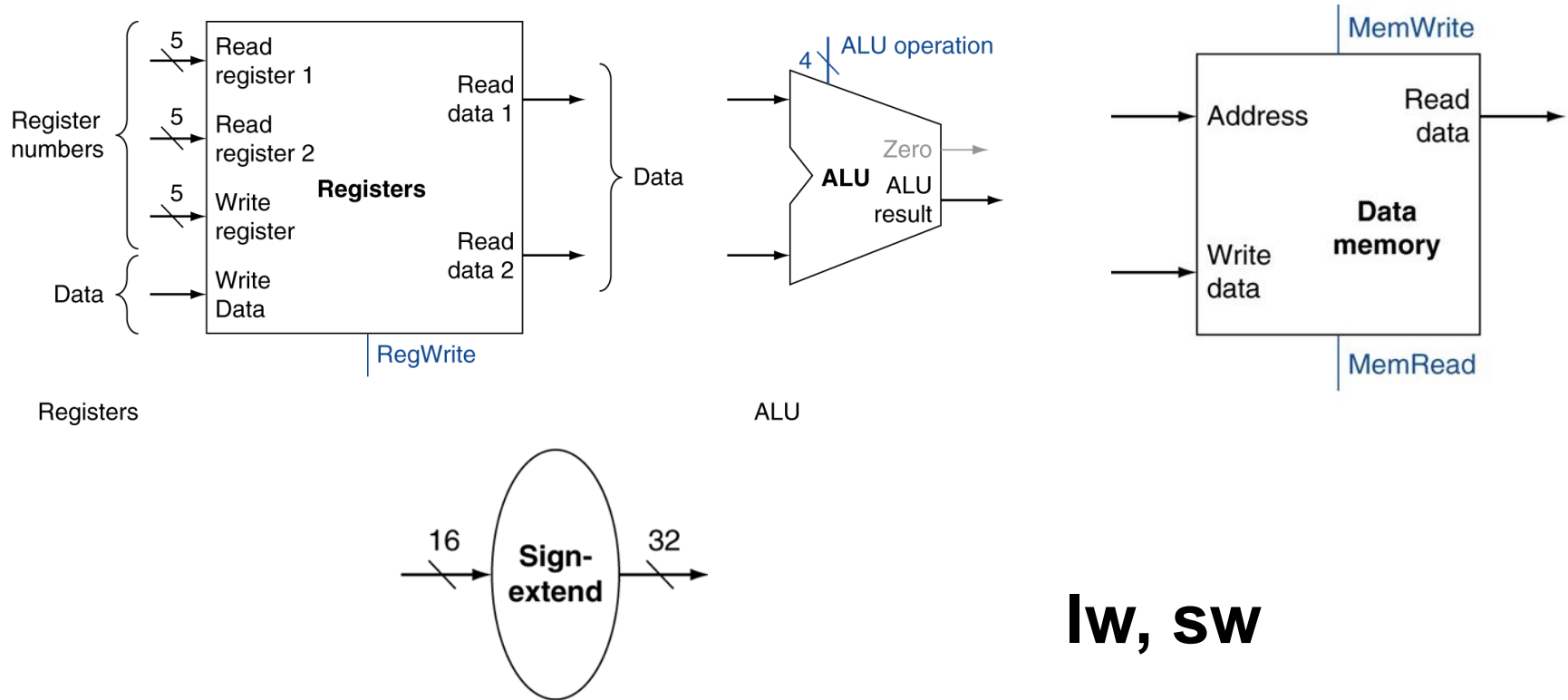


# Datapath for a Branch

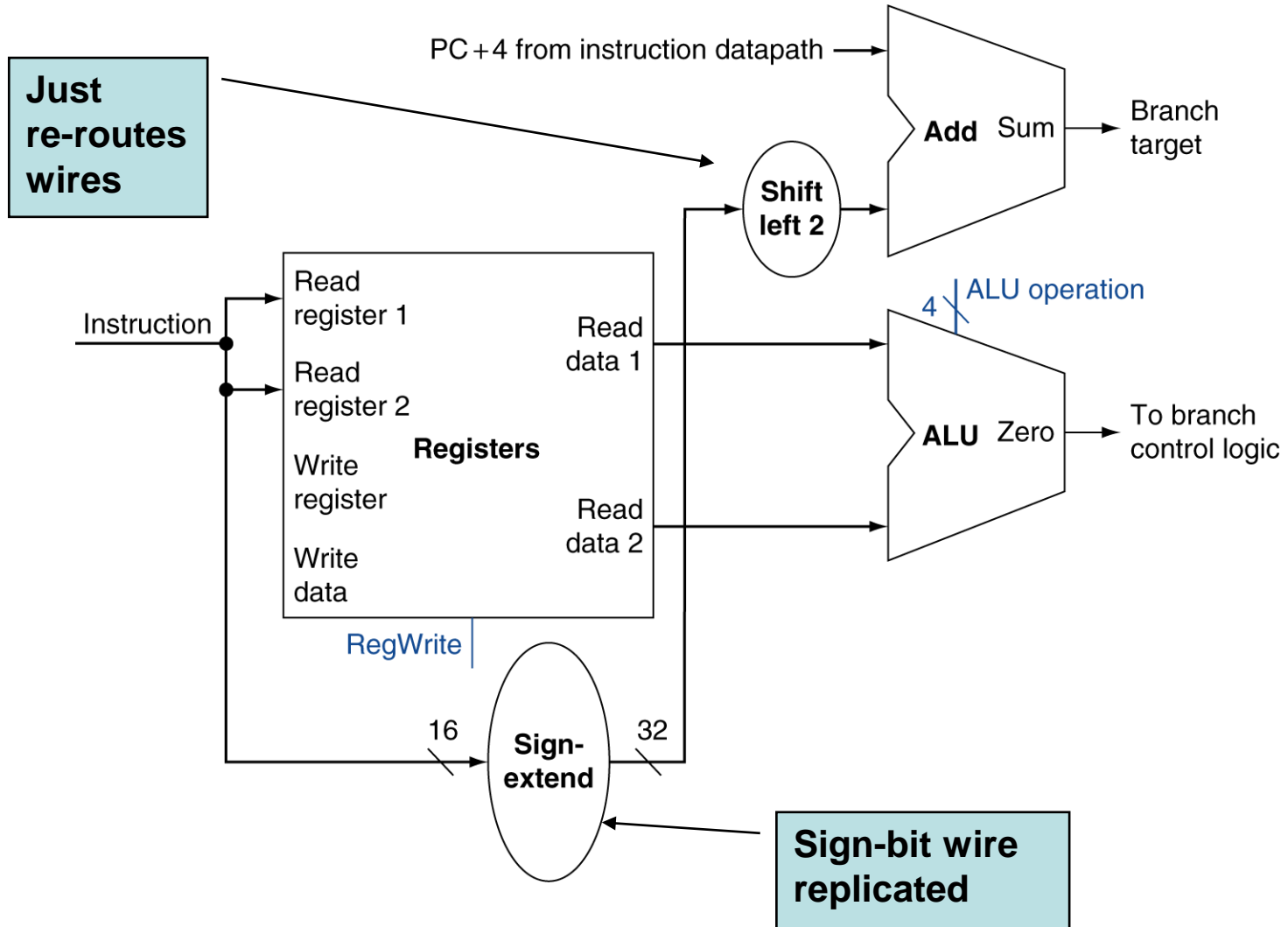


# R-type + (Load or Store)

- Need two extra multiplexers.

 
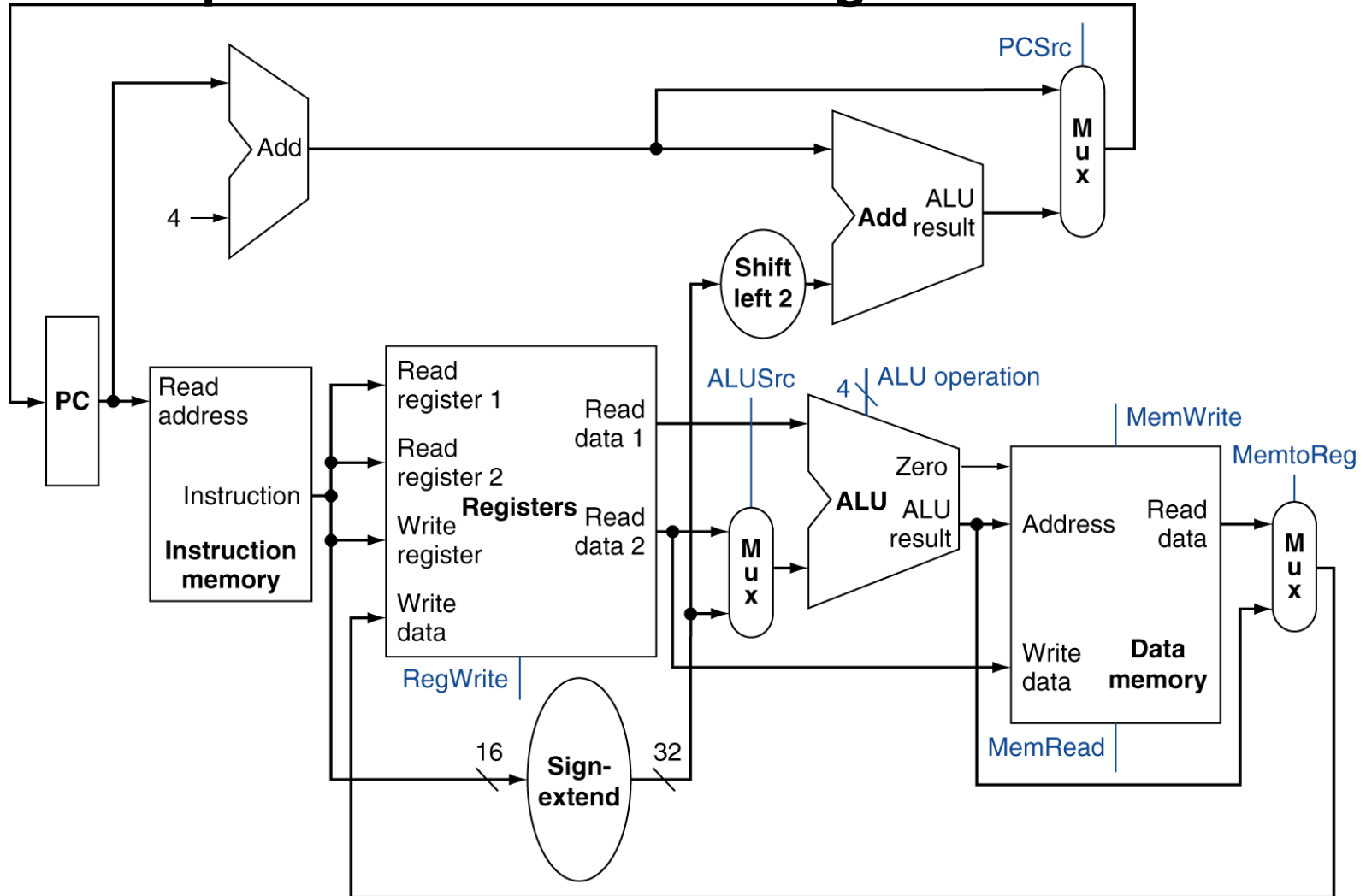
# R-type + (Load / Store) + Branch + PC

- Use multiplexers to stitch them together



A close-up image of a microchip or integrated circuit, showing its square shape and numerous pins.

# Summary

- **We have built datapath for single clock cycle datapath. The components are arranged so that data can flow through them to produce correct output.**

# 1. Review

- Logic design review
- MIPS instruction review

# 2. Building Datapath

# 3. A Simple Implementation Scheme



# Introduction


- **In this section we will learn control signals for datapath built in previous section.**
- **We will also see how data flows MIPS CPU for each MIPS instruction.**
- **Also we will try to measure its performance.**



# Operation/Instruction Format Summary


- **Add, sub, and, or**

- `add rd, rs, rt`
- `and rd, rs, rt`

 

- **Load, store**

 - `lw rt, rs, imm16`
- `sw rt, rs, imm16`




- **Branch**

- `beq rs, rt, imm16`

# R-type + (Load or Store) + Branch + PC

- More multiplexer...

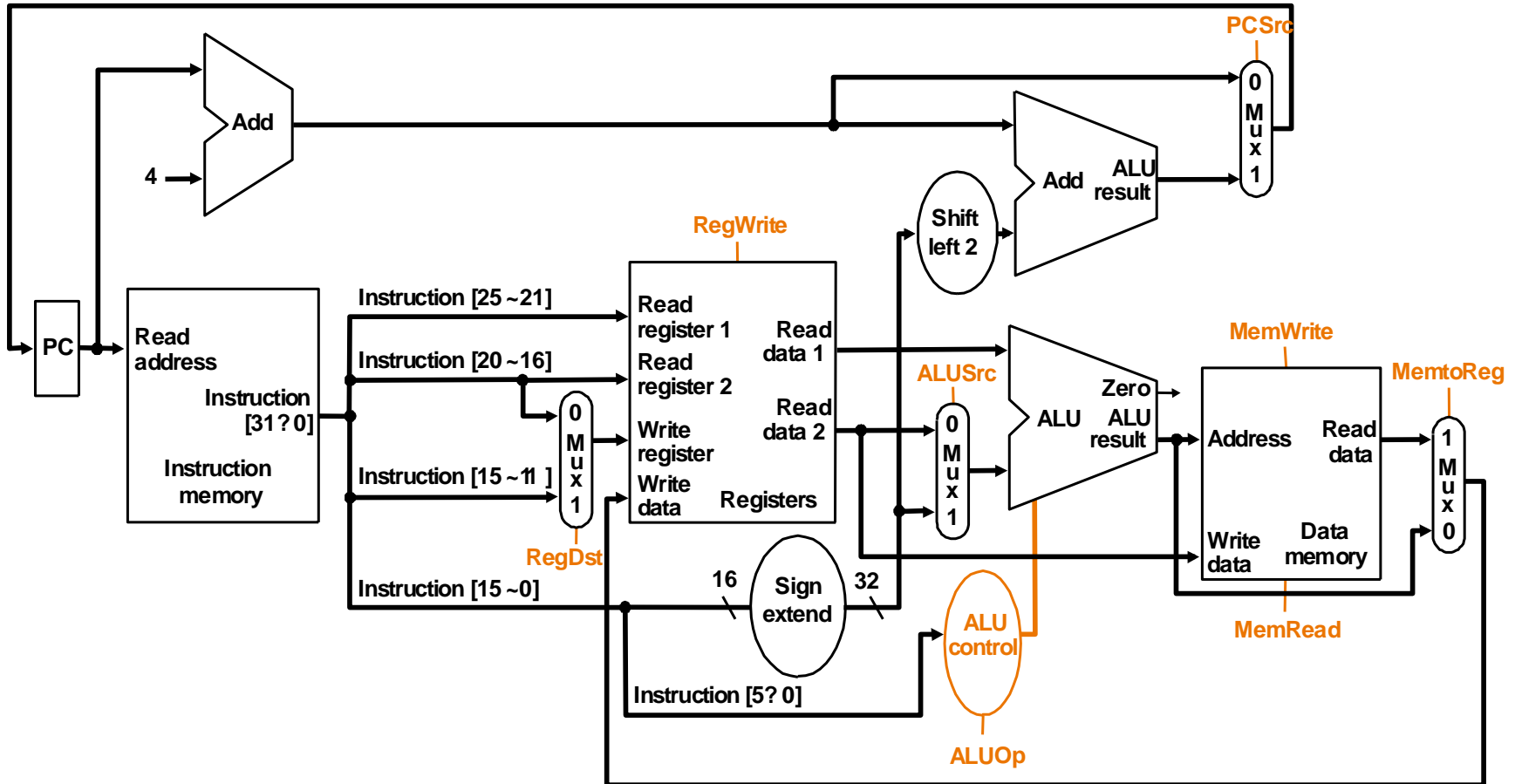

# Detailed Design of Control

- **Control Signal Types**
  - Selecting the operations to perform (ALU, read/write, etc.)
  - Controlling the flow of data (selecting multiplexer inputs)
- **Information comes from the 32 bits of the instruction**
- **Example: add \$8, \$17, \$18 Instruction Format:**

add    

000000	10001	10010	01000	00000	100000
--------	-------	-------	-------	-------	--------

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

and    

000000					100100
--------	--	--	--	--	--------

or    

000000					100101
--------	--	--	--	--	--------

sub    

000000					100010
--------	--	--	--	--	--------

slt    

000000					101010
--------	--	--	--	--	--------

- ALU operation is based on **op. code and function code**

# Detailed Design of Control : ALU Control

- e.g., what should the ALU do with this instruction

Example: lw \$1, 100(\$2)

35	2	1	100
op	rs	rt	16 bit offset


lw	100011			
sw	101011			
beq	000100			

Need 'add' op.

Need 'add' op.

Need 'sub' op.


ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

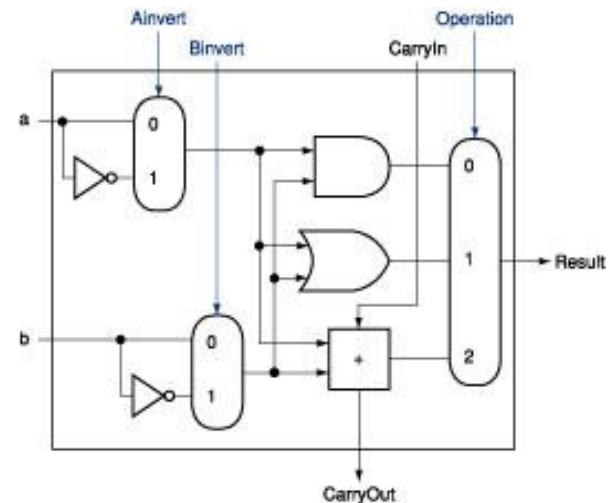
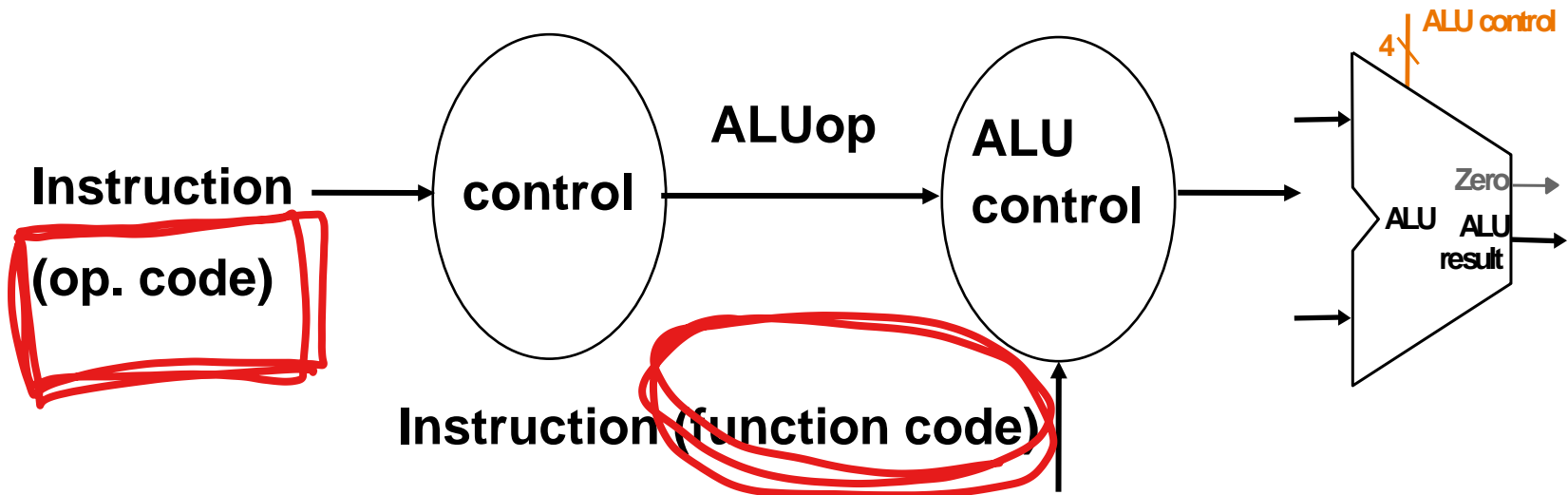
# Detailed Design of Control : ALU Control

- output : 4-bit **ALU control** input
- input :
  - **ALUOp** from 'control' component
    - 00 = lw, sw
    - 01 = beq,
    - 10 = arithmetic

} ALUOp computed from op. code in instruction
  - **function code** for arithmetic



# Detailed Design of Control : ALU Control

- Describe it using a truth table (can be turned into gates):

ALUOp		Function field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
lw, sw beq	0	X	X	X	X	X	X	0010
	X	X	X	X	X	X	X	0110
R-format (add,sub, and,or,slt)	1	X	X	0	0	0	0	0010
	1	X	X	0	0	1	0	0110
	1	X	X	0	1	0	0	0000
	1	X	X	0	1	0	1	0001
	1	X	X	1	0	1	0	0111

# ALU control signal and its action

*Arithmetic*


Instruction opcode	ALUOp	Instruction Operation	Function field	Desired ALU action	ALU control Input
LW	00	load word	XXXXXXX	add	0010
SW	00	store word	XXXXXXX	add	0010
Branch equal	01	branch equal	XXXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

# Control Signals

Signal name	Effect when disserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the rt field (bits 20:16)	The register destination number for the Write register comes from the rd field (bits15:11)
RegWrite	None.	The register on the Write register input is written with the value on the Write data Input
ALUSrc	The second ALU operand comes from the second register file output (Read data2)	The second ALU operand is the sign-extended, lower 16 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of PC +4	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input
MemtoReg	The value fed to the register Write data input comes from the ALU	The value fed to the register Write data input comes from the data memory




# With Control Unit

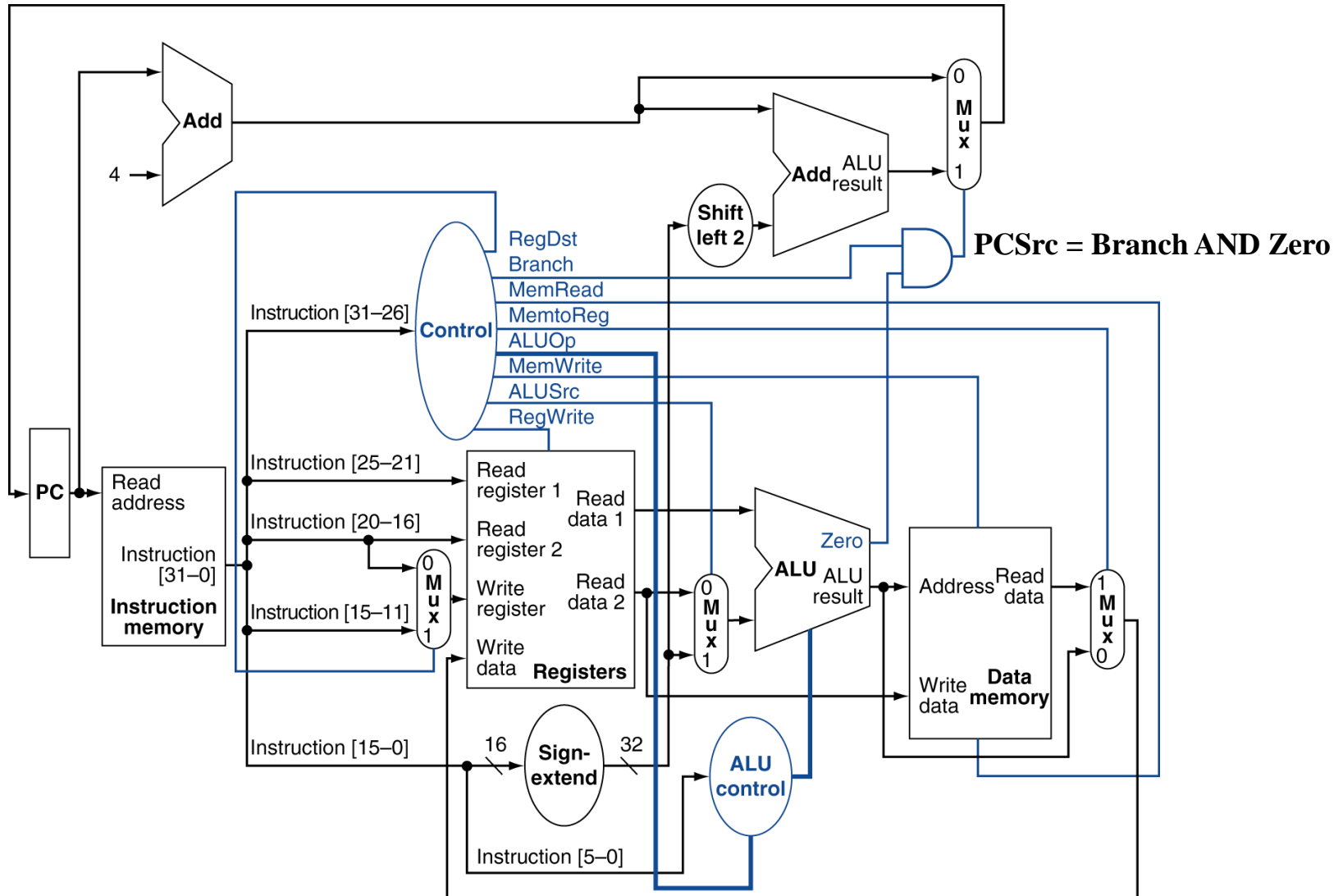

# Detailed Design of Control

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp 1	ALUOp 0
<b>R-format</b>									
lw									
sw									
beq									

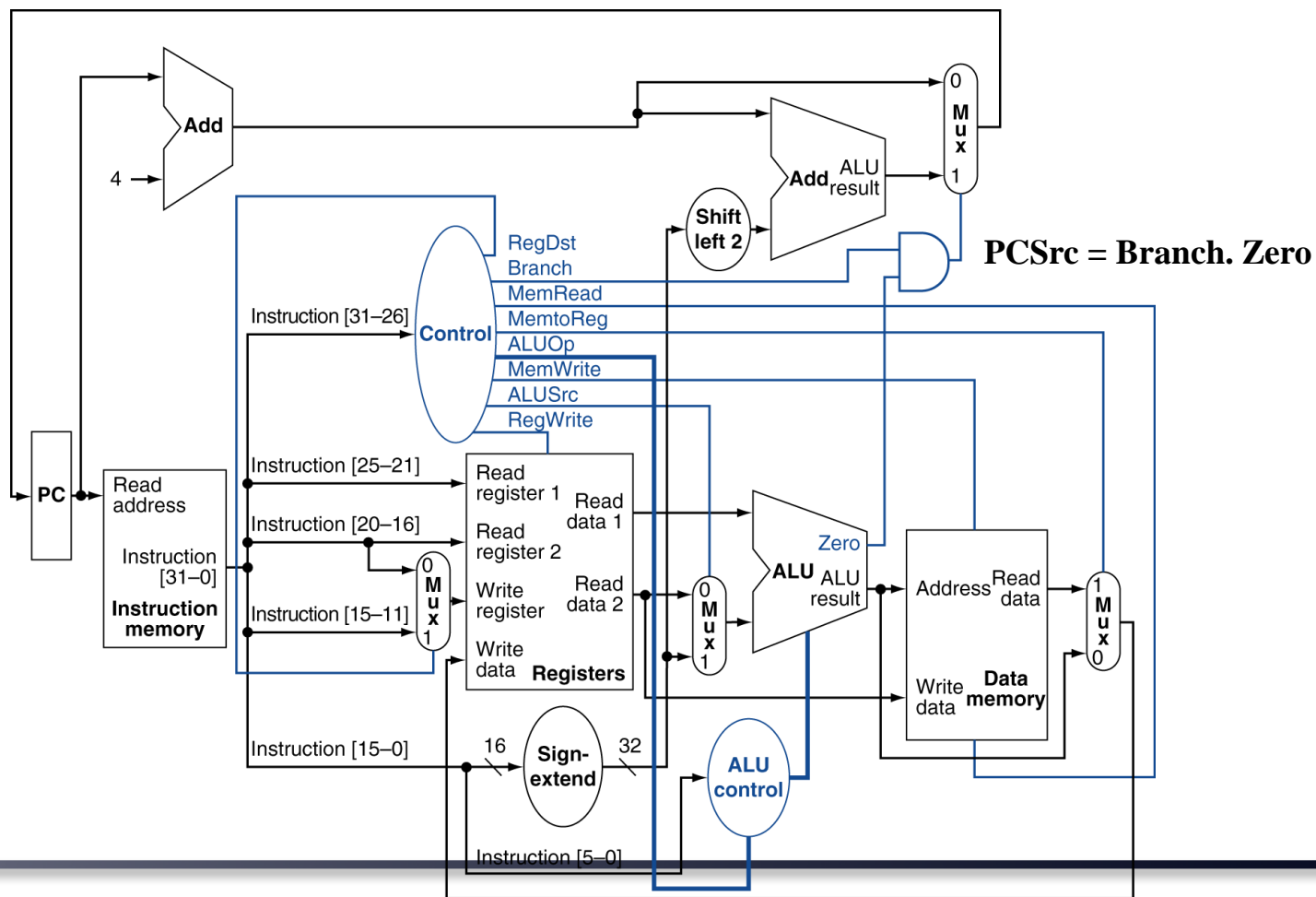



# A Simple Cycle Implementation

**= A single clock implementation**

- All instructions are executed in one clock cycle.**


**Thus, no resource can be used more than once per instruction.**

**→ need separate instruction and data memory.**

**need several adders.**
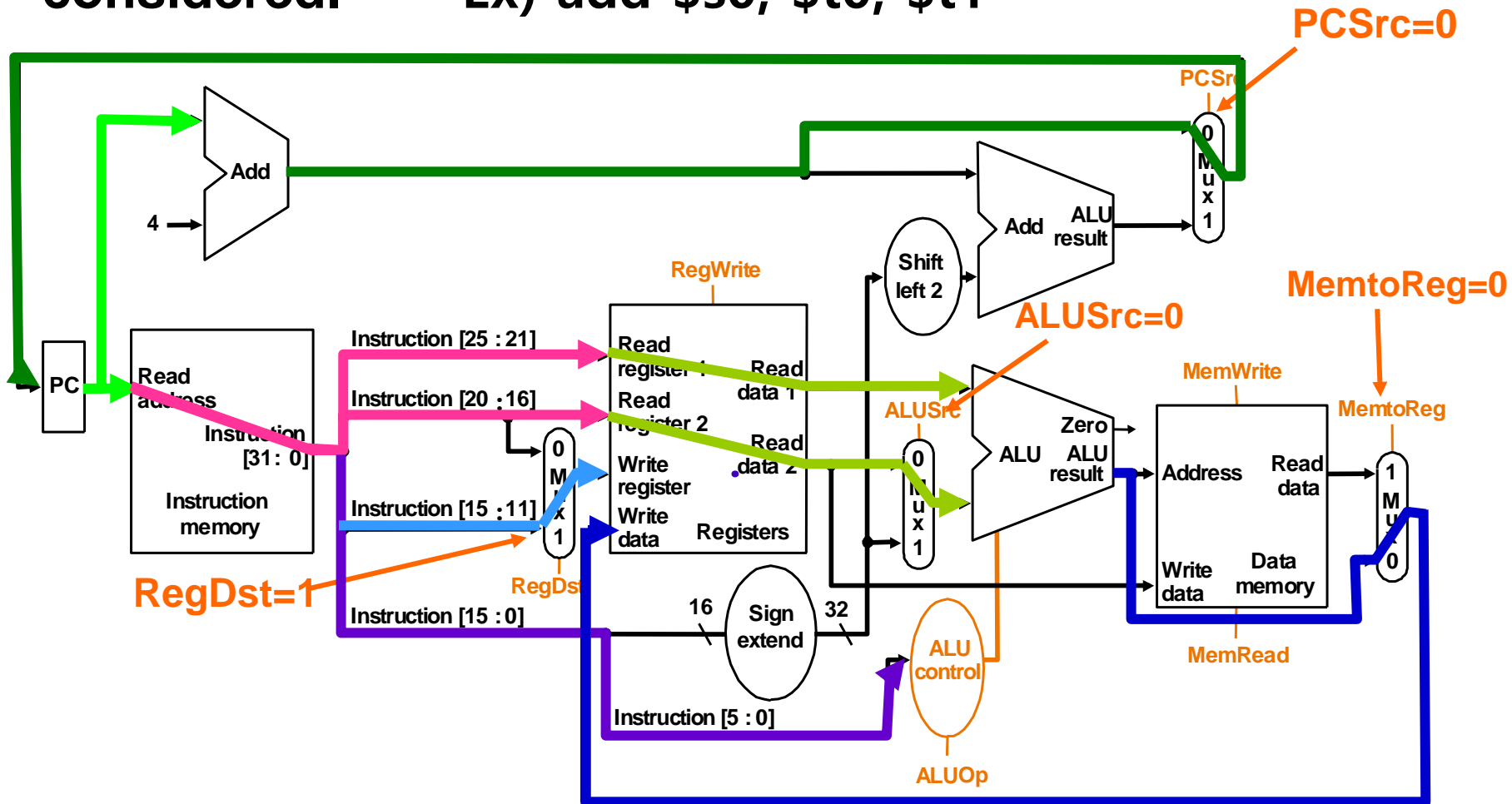
# R-format instructions dataflow

- Only 'add', 'sub', 'and', 'or', and 'slt' instructions are considered. Ex) add \$s0, \$t0, \$t1



# R-format Operation Control

- We thus have the following control signals for these ops:


RegDst	1 to select Rd
RegWrite	1 to enable writing Rd
ALUSrc	0 to select Rt value from register file
ALUOp	<i>Dependent on operation</i> (see below)
MemWrite	0 to disable writing memory
MemRead	0 to disable reading memory
MemtoReg	0 to select ALU output to register
PCSrc	0 to select next PC

- The ALU requires control based on the op:

add	OP(add)	and	OP(and)
sub	OP(sub)	or	OP(or)
slt	OP(slt)		

# I-format 'Load' instruction dataflow

lw \$s0, 100(\$t0)

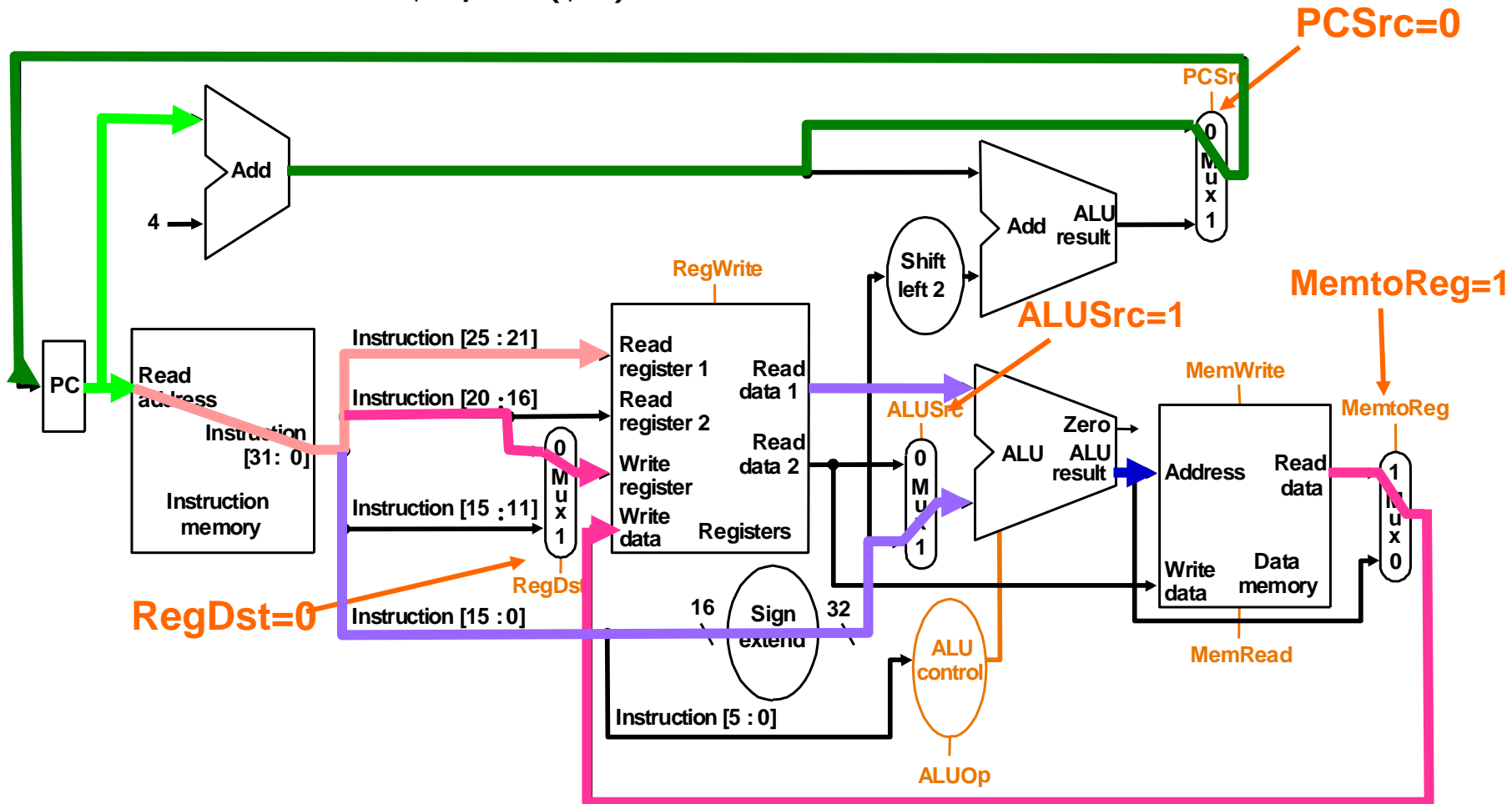


# I-format Load Operation Control

- We thus have the following control signals for these ops:

RegDst	0 to select Rt
RegWrite	1 to enable writing Rt
ALUSrc	1 to select immediate field value from instruction
ALUOp	add
MemWrite	0 to disable writing memory
MemRead	1 to enable reading memory
MemtoReg	1 to select memory output to register
PCSrc	0 to select next PC

# I-format 'Store' instruction dataflow

sw \$s0, 100(\$t0)

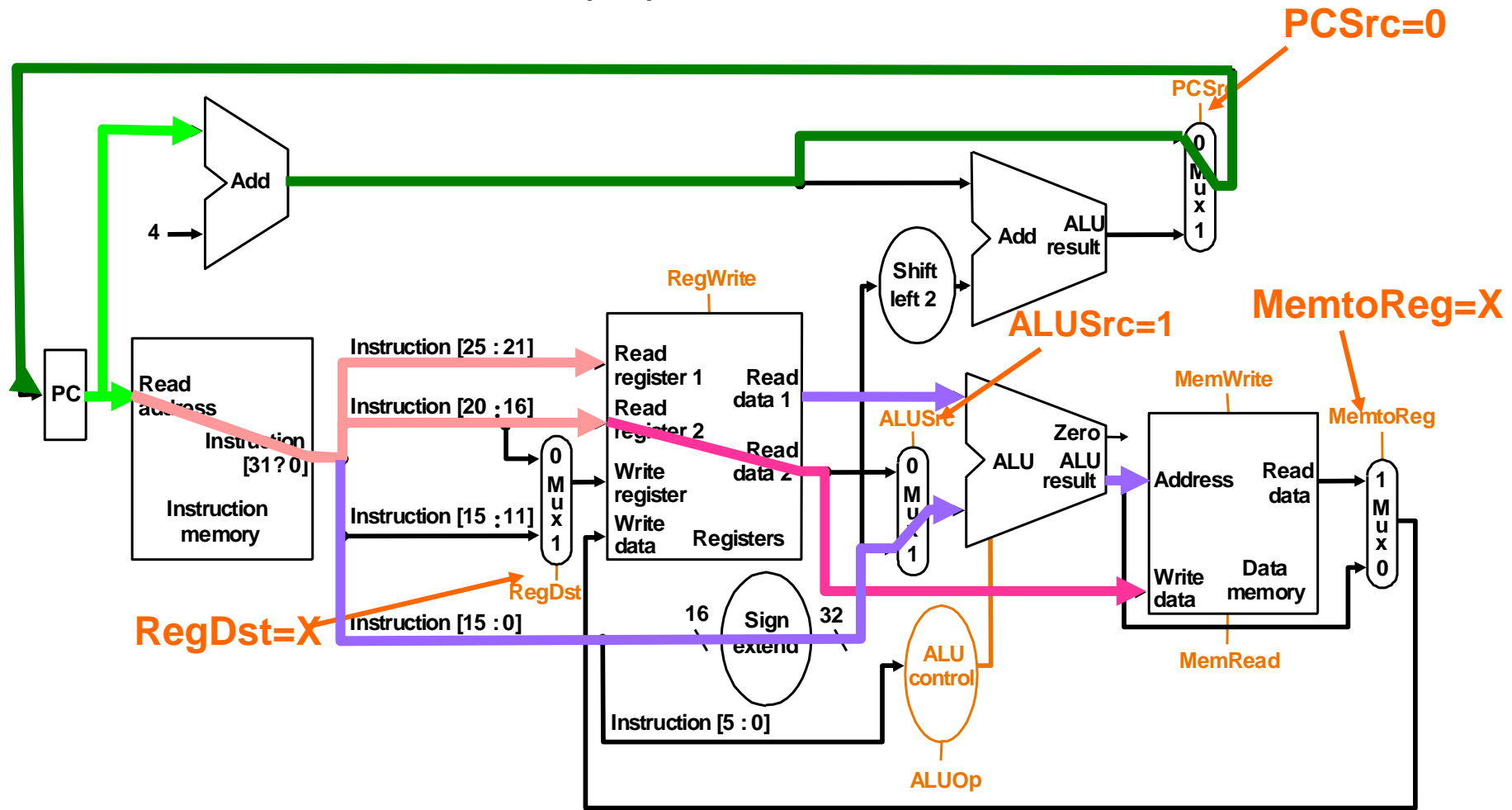




# I-format Store Operation Control

- We thus have the following control signals for these ops:

RegDst	X (don't care)
RegWrite	0 to disable writing a register
ALUSrc	1 to select immediate field value from instruction
ALUOp	add
MemWrite	1 to enable writing memory
MemRead	0 to disable reading memory
MemtoReg	X (don't care)
PCSrc	0 to select next PC

# I-format 'Beq' instruction dataflow

beq \$s0, \$s1, loop

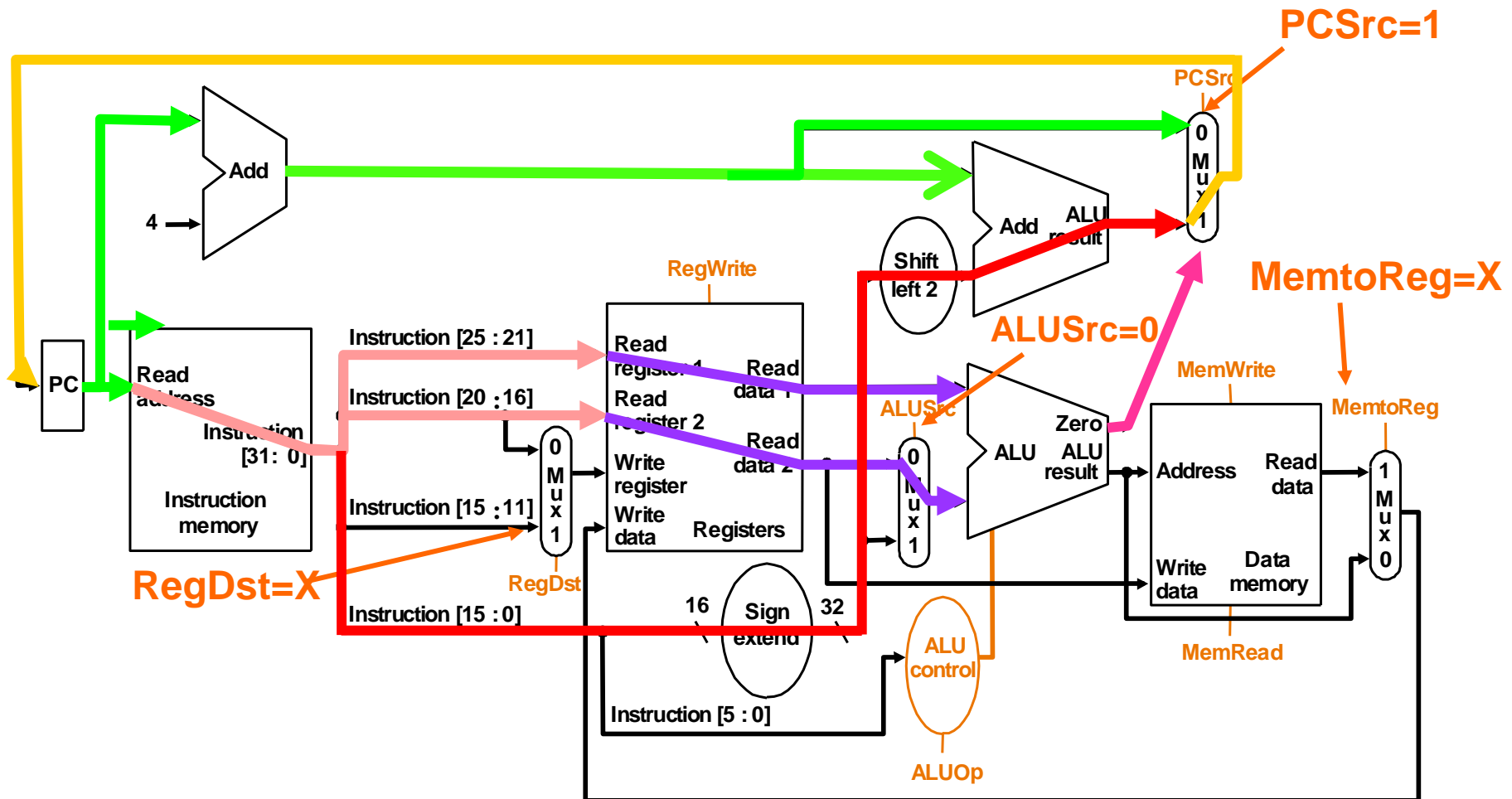

# I-format Branch Operation Control

- We thus have the following control signals for these ops:

RegDst	X (don't care)
RegWrite	0 to disable writing a register
ALUSrc	0 to select Rt value from register file
ALUOp	sub
MemWrite	0 to disable writing memory
MemRead	0 to disable reading memory
MemtoReg	X (don't care)
PCSrc	zero AND branch

# Single-cycle Control Signals Summary

- From the preceeding analyses, we have the following control signals required:

<u>Signal</u>	<u>R-fmt</u>	<u>I-fmt (lw)</u>	<u>I-fmt (sw)</u>	<u>I-fmt (beq)</u>
RegDst	1	0	x	x
RegWrite	1	1	0	0
ALUSrc	0	1	1	0
ALUOp	OP	add	add	sub
MemWrite	0	0	1	0
MemRead	0	1	0	0
MemtoReg	0	1	x	x
PCSrc	0	0	0	zero

- Note that the only time that the PCSrc signal is active is during a branch, thus


$$PCSrc = (\text{Operation is a branch}) \wedge \text{zero}$$

# Adding Jump Implementation ?

000010

address(26-bits)


Target = PC(31:28) && (address << 2)

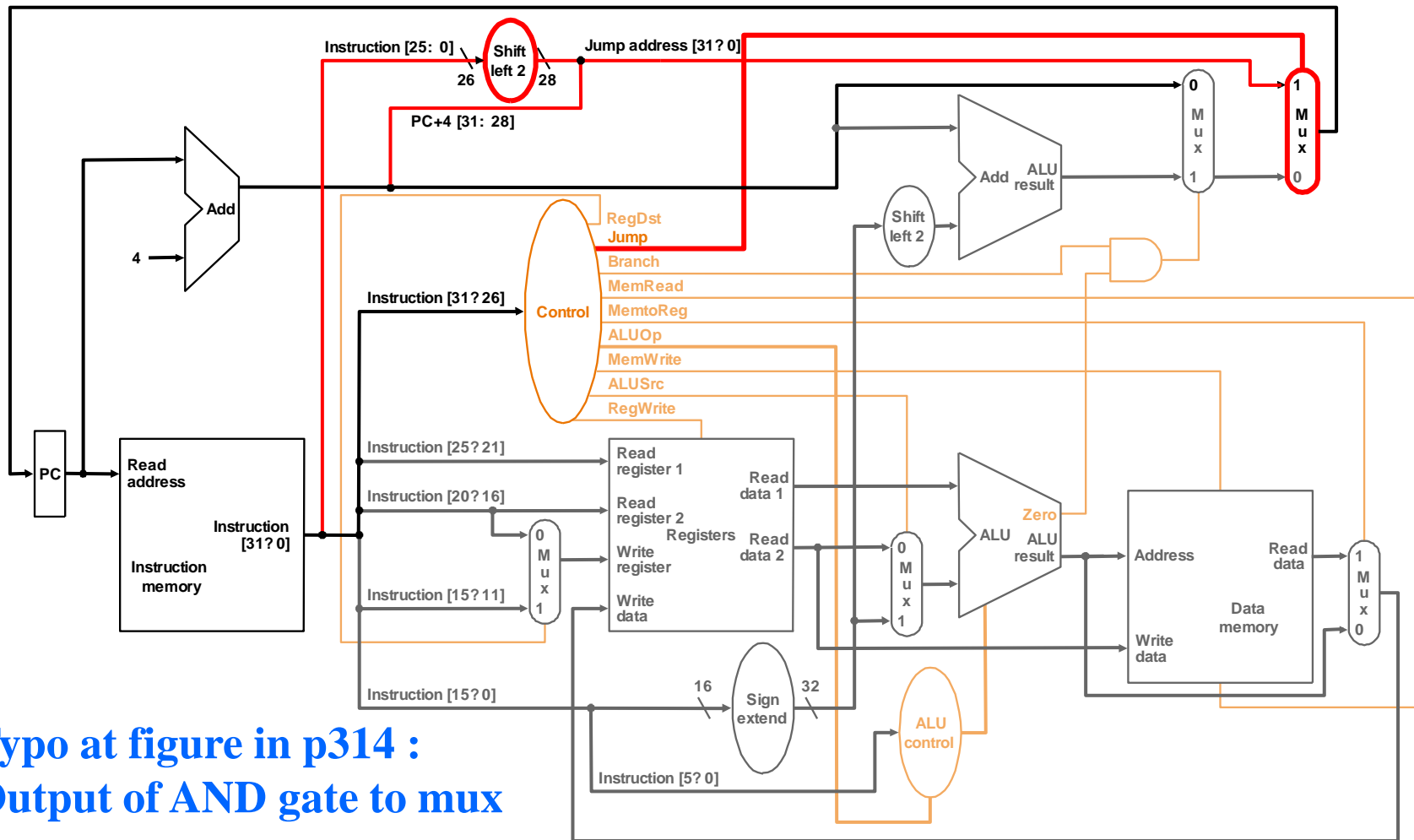

Typo at figure in p314 :  
Output of AND gate to mux

 
# Our Single Cycle Control Structure

- All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
  - ALU might not produce right answer right away
  - We use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path



*We are ignoring some details like setup and hold times*

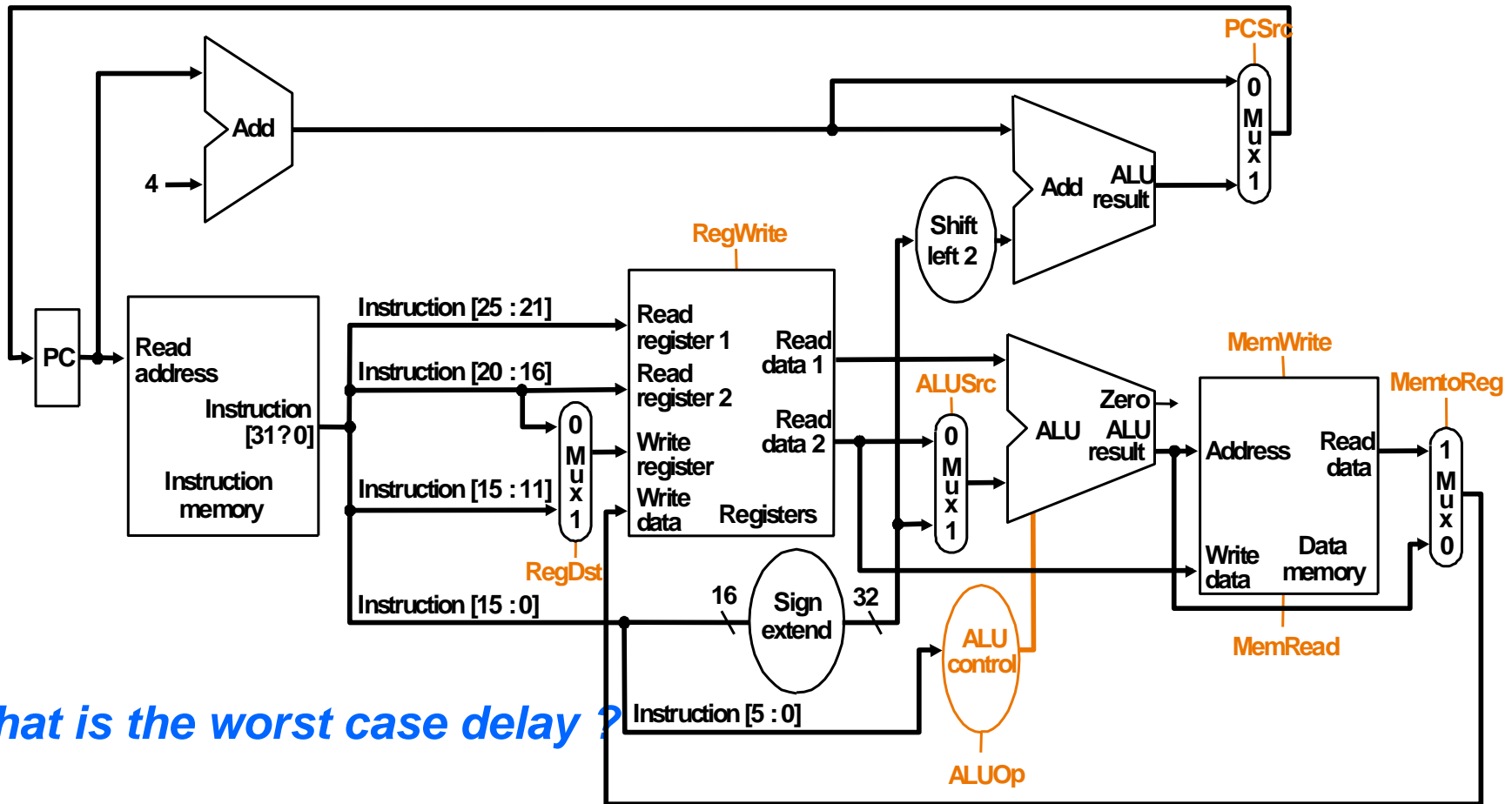- **Calculate cycle time assuming negligible delays except:**
  - memory (200ps), ALU and adders (100ps), register file access(50ps)



## What is the worst case delay ?


# Single Cycle Implementation Performance

instruction class	Functional units used by the instruction class				
ALU type	Instr. Fetch (200ps)	register access (50ps)	ALU (100ps)		register access (50ps)
Load word	Instr. Fetch (200ps)	register access (50ps)	ALU (100ps)	Memory access(200ps)	register access (50ps)
Store word	Instr. Fetch (200ps)	register access (50ps)	ALU (100ps)	Memory access(200ps)	
Conditional Branch	Instr. Fetch (200ps)	register access (50ps)	ALU (100ps)		
Jump	Instr. Fetch (200ps)				

- The Clock Cycle time with single clock will be determined by the longest instruction, which is **600 ps**
- $CPI = 1$
- $Execution\ Time = instruction\# * CPI * Clock\ Cycle\ Time$   
 $= instruction\# * 600\ ps$



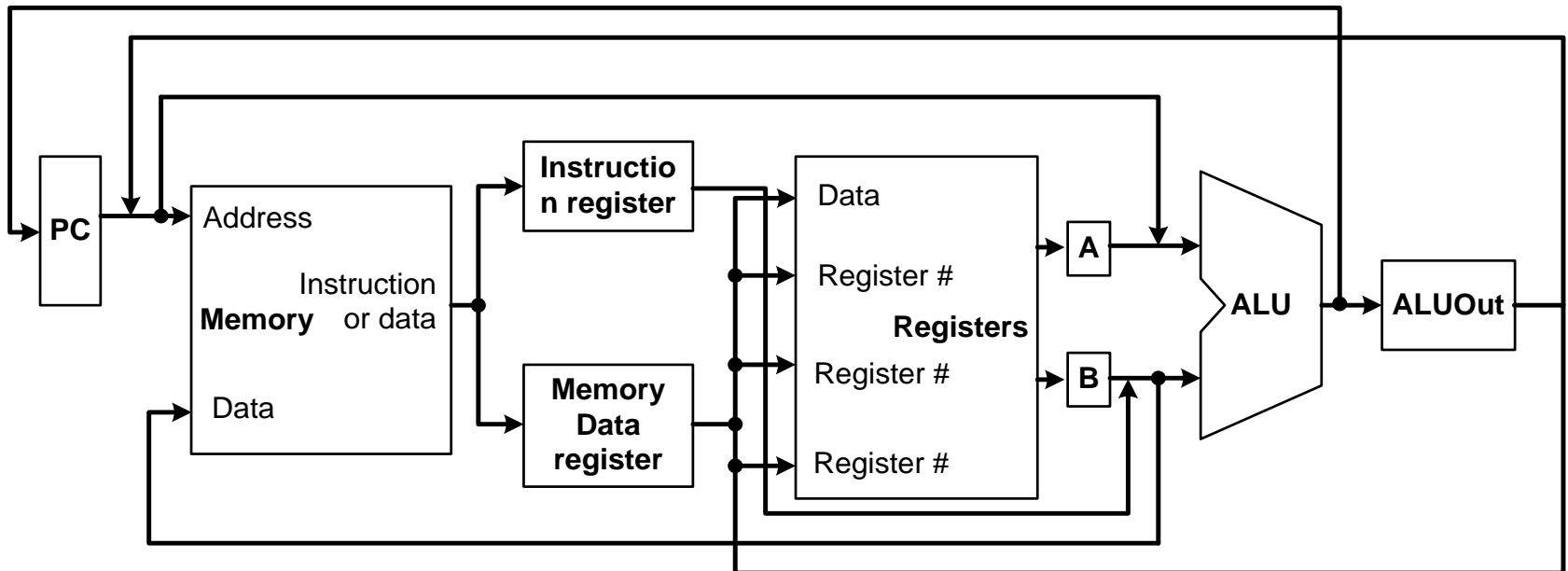- **Single Cycle Problems:**
  - what if we had a more complicated instruction like floating point?
  - waste of chip area
- **One Solution:**
  - Make cycle time smaller & have different instructions take different numbers of cycles → a multicycle datapath:



# Summary

- We verified the MIPS datapath built in previous section executes MIPS instruction correctly.
- Different instruction takes different amount of time to be executed, which gives a room for performance improvement.

# 1. Review

- Logic design review
- MIPS instruction review

# 2. Building Datapath

# 3. A Simple Implementation Scheme

# 4. Multicycle Implementation



# Introduction

- In this section the datapath in previous section is modified to build multi-clock cycle datapath.
- In multicycle datapath, it takes several clock cycles to execute one instruction.
- We need extra components to build multicycle datapath.




# Multicycle Approach


- We will be **reusing functional units**
  - **ALU** used to compute address and to increment PC
  - **Memory** used for instruction and data
- We'll use a **finite state machine** for control
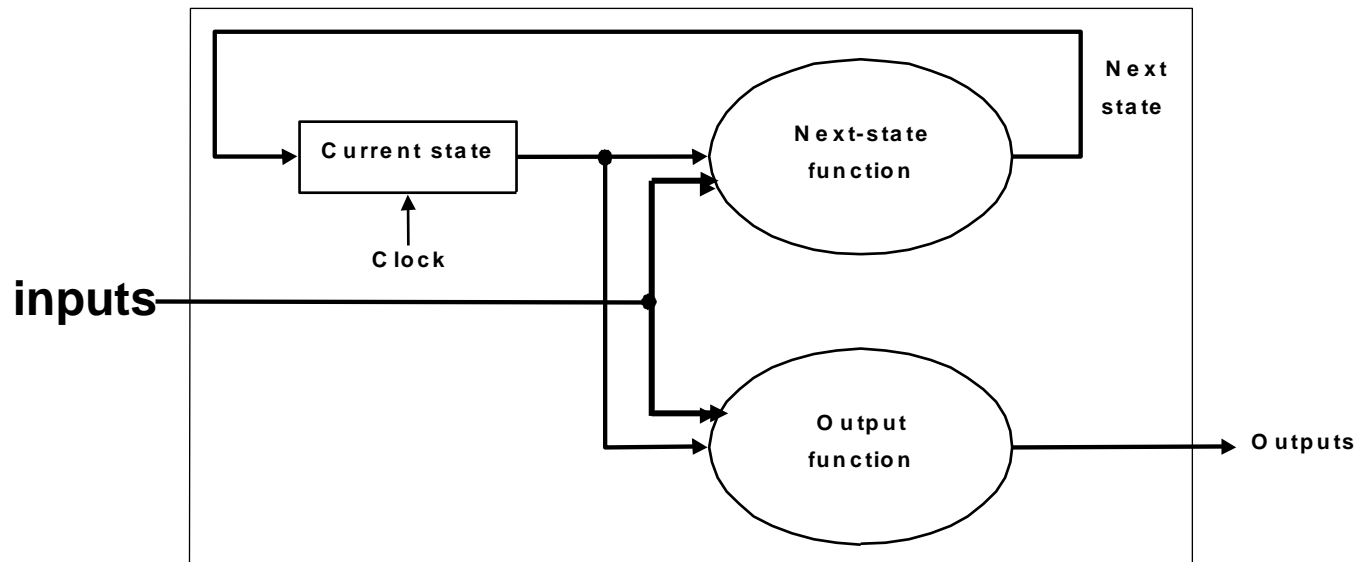
# Review: finite state machines

- **Finite state machines:**
  - a set of states and
  - next state function (determined by current state and the input)
  - output function (determined by current state and possibly input)




- **We'll use a Moore machine (output based only on current state)**



# MultiCycle Datapath for MIPS

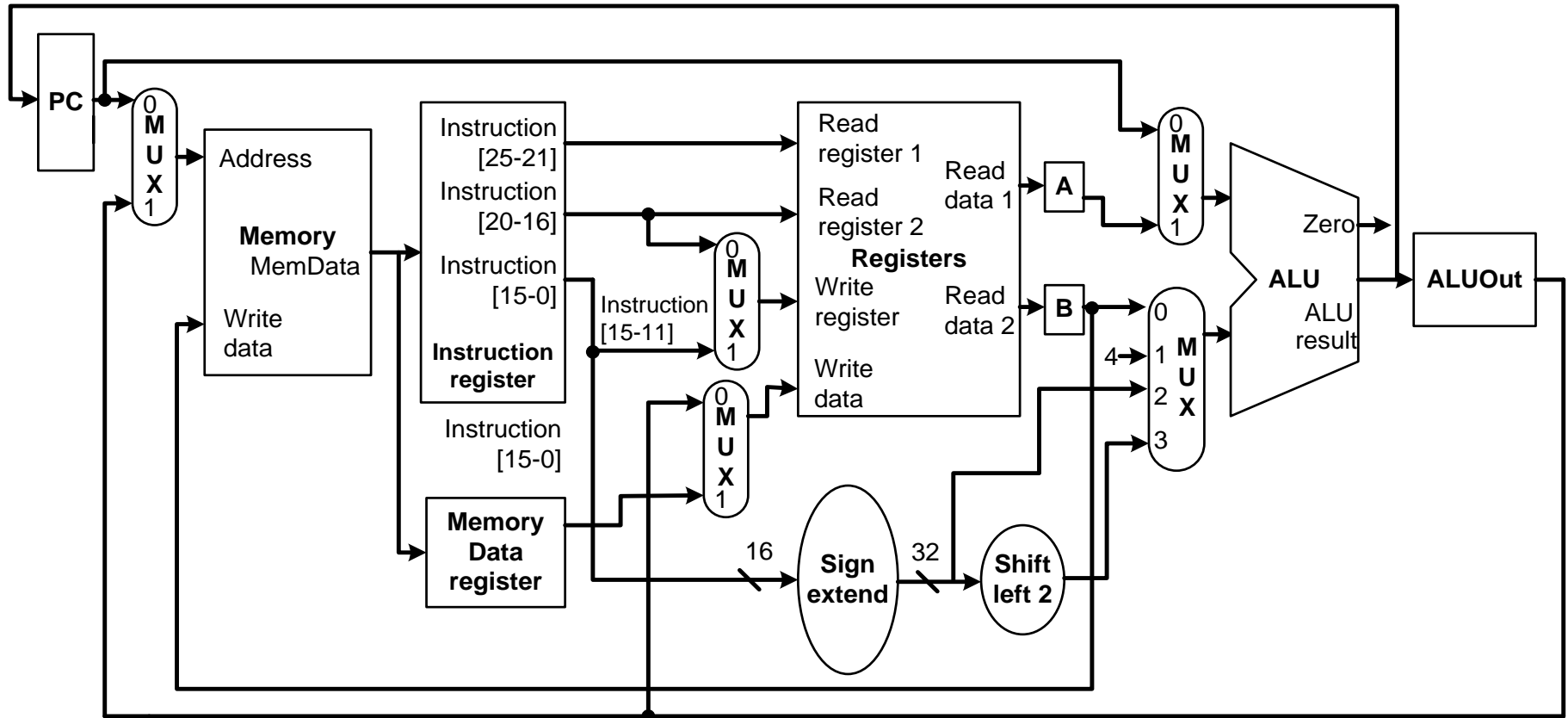
## Basic Instructions

- **Break up the instructions into steps, each step takes a cycle**
  - balance the amount of work to be done
  - restrict each cycle to use only one major functional unit
- **At the end of a cycle**
  - store values for use in later cycles (easiest thing to do)
  - introduce additional internal registers





# Multicycle datapath

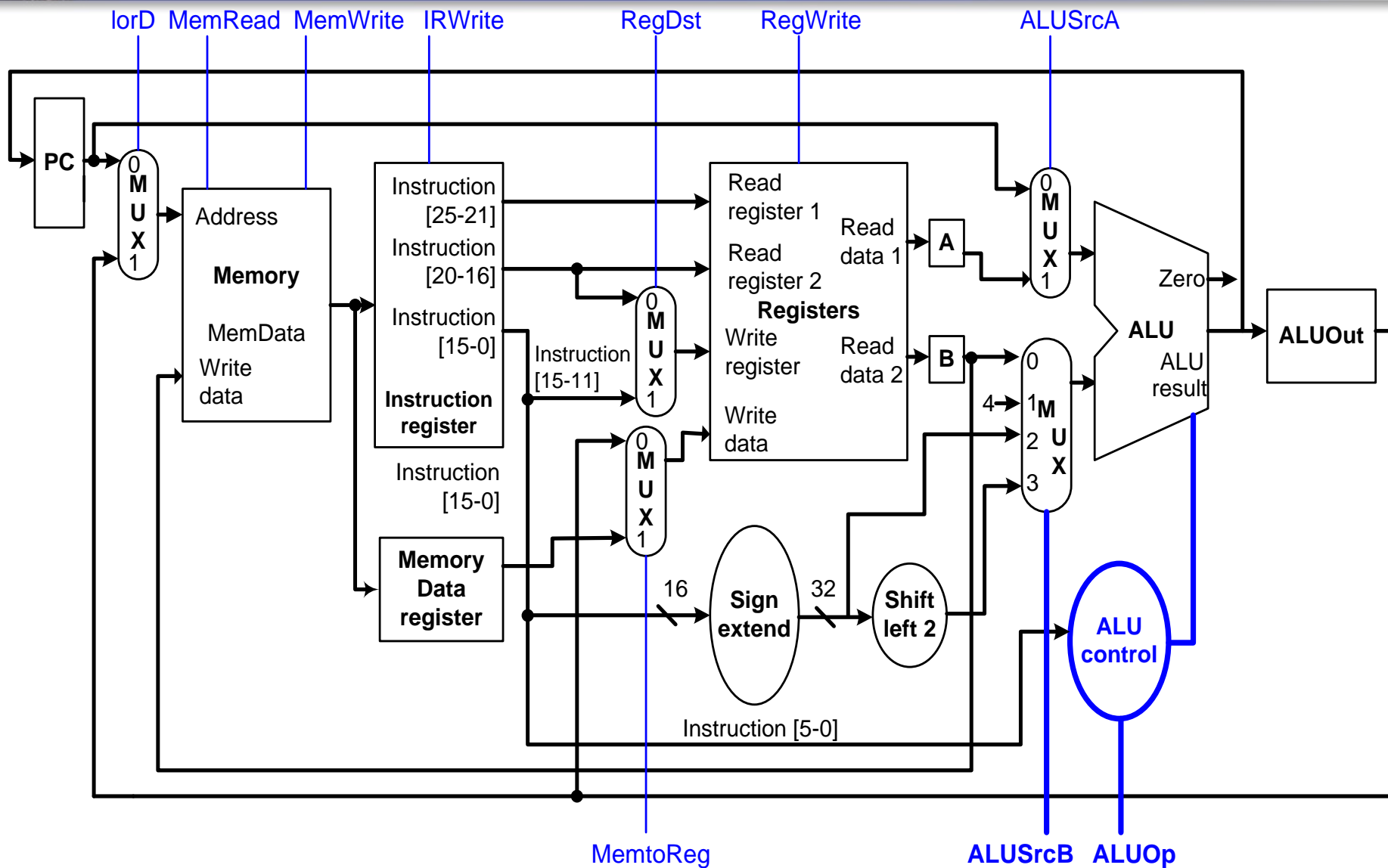



# Comparing simplecycle datapath with multicycle datapath

- **Single Memory**
- **Single ALU**
- **Several registers are added to store intermediate results**
  - Instruction Register
  - A, B
  - ALUout
  - Memory Data Register      cf) Memory Address Register
- **We need more multiplexers to share functional units.**
  - Mux in front of memory
  - Muxes in front of ALU



# Five Execution Steps

- 1. Instruction Fetch**
- 2. Instruction Decode and Register Fetch**
- 3. Execution, Memory Address Computation, or Branch Completion**
- 4. Memory Access or R-type instruction completion**
- 5. Write-back step**

***INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!***

# Step 1: Instruction Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR <= Memory[PC] ;  
PC <= PC + 4 ;
```

*Can we figure out the values of the control signals?*


*What is the advantage of updating the PC now?*

# Instruction Fetch

## ● RTL Description

$IR \leftarrow \text{Memory}[PC];$

$PC \leftarrow PC + 4;$

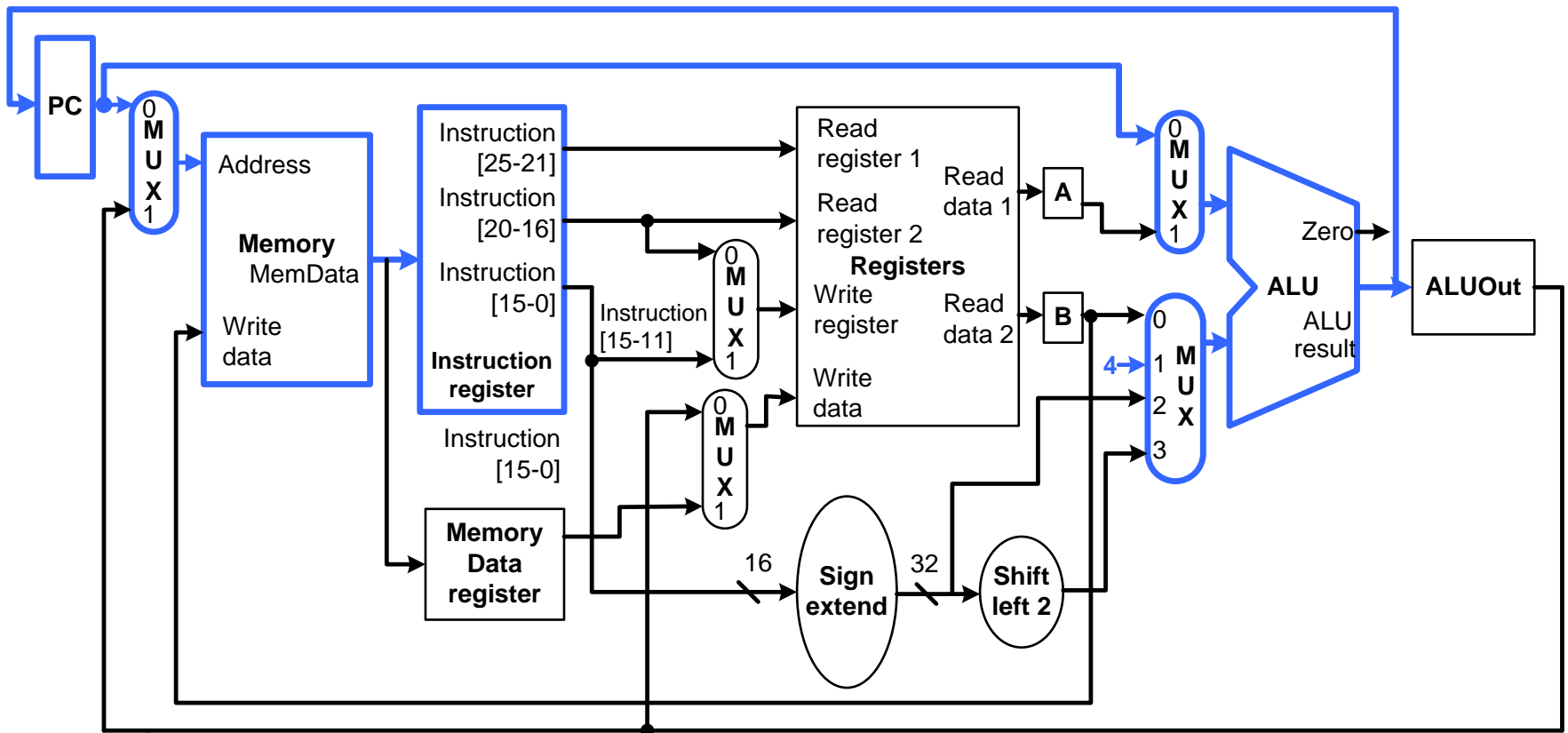

## Step 2: Instruction Decode and Register Fetch

- Read registers rs and rt in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:
  - `A <= Reg[IR[25-21]] ;`
  - `B <= Reg[IR[20-16]] ;`
  - `ALUOut <= PC + (sign-extend(IR[15-0]) << 2) ;`
- We aren't setting any control lines based on the instruction type  
(we are busy "decoding" it in our control logic)

# Instruction Decode and Register Fetch


## RTL Description

$A \leftarrow \text{Reg}[\text{IR}[25-21]];$

$B \leftarrow \text{Reg}[\text{IR}[20-16]];$

$\text{ALUOut} \leftarrow \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2);$

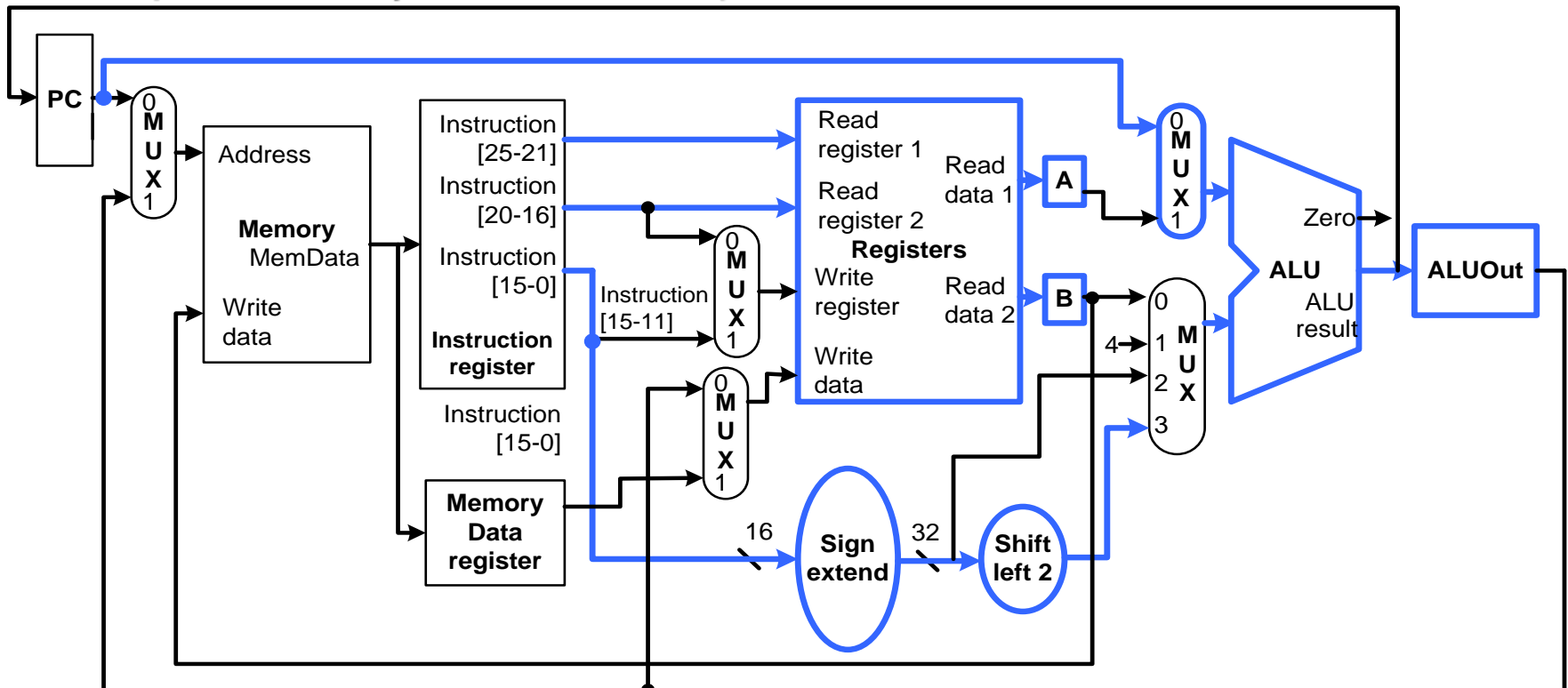—The ALU is used to calculate the branch destination speculatively in case the operation is, in fact, a branch




## Step 2: Instruction Decode and Register Fetch

- Computing the branch target address is not going to be used in next step if the instruction is not branch. However, it is not harmful doing so at this stage. :

Optimistic approach

 - Control signals are not determined by instruction in this step. (The control signals in step 1 & 2 are same regardless of instruction type.)





## Step 3: Instruction dependent

- ALU is performing one of three functions, based on instruction type
- Memory Reference:

`ALUOut <= A + sign-extend(IR[15-0]);`

- R-type:

`ALUOut <= A op B;`

- Branch:

`if (A==B) PC <= ALUOut;`

## Step 4: R-type or memory-access

- Loads and stores access memory

`MDR <= Memory[ALUOut] ;`

`or`

`Memory[ALUOut] <= B ;`

- R-type instructions completion

`Reg[IR[15-11]] <= ALUOut ;`




## Step 5: Memory read completion step

- `Reg[IR[20-16]] <= MDR;`

*What about all the other instructions?*
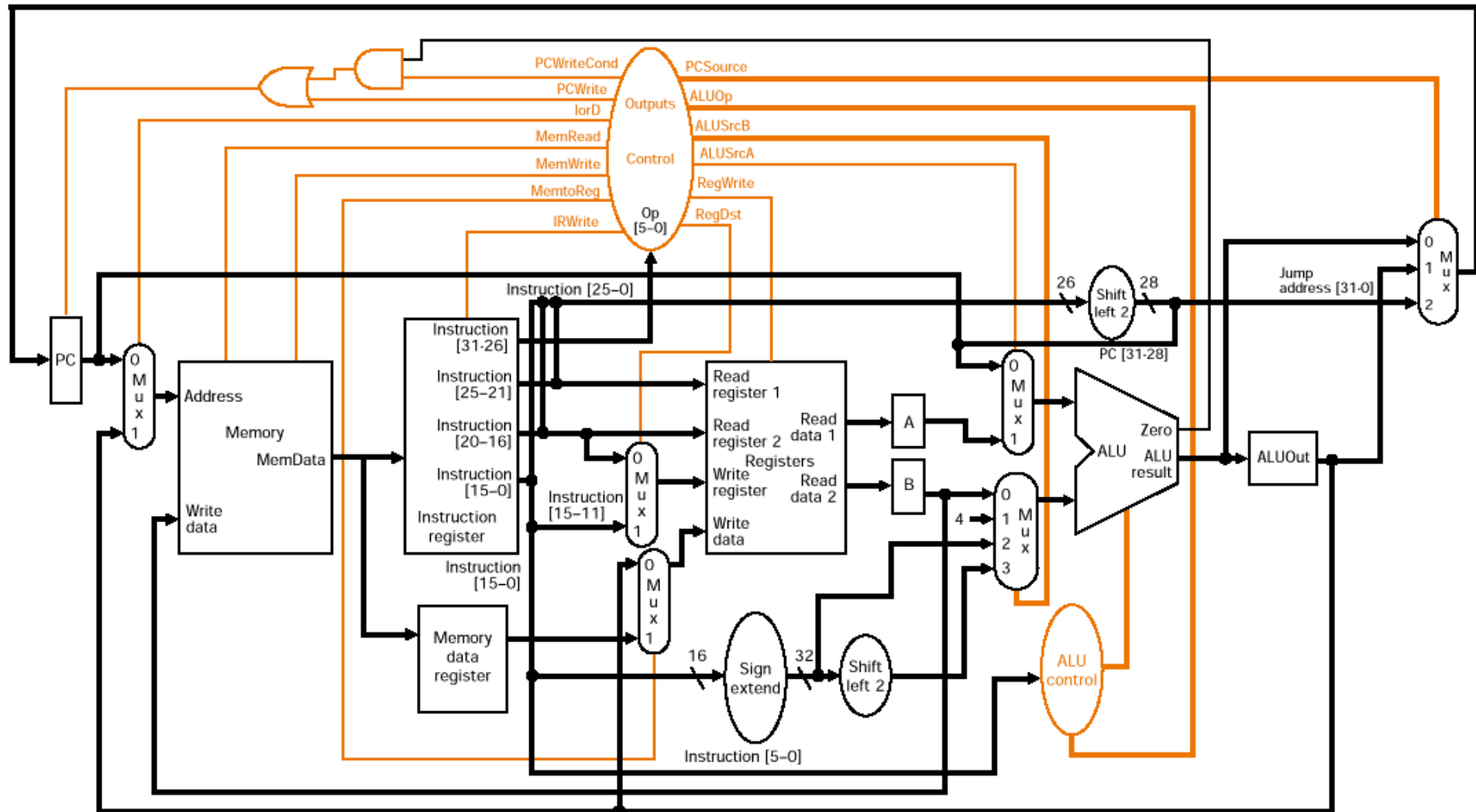
# Multicycle Implementation (including 'jump' instruction & Control Unit)



# Summary

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR = \text{Memory}[PC]$ $PC = PC + 4$			
Instruction decode/register fetch	$A = \text{Reg}[IR[25-21]]$ $B = \text{Reg}[IR[20-16]]$ $ALUOut = PC + (\text{sign-extend-to32}(IR[15-0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut = A \text{ op } B$	$ALUOut = A + \text{sign-extend}(IR[15-0])$	if $(A == B)$ then $PC = ALUOut$	$PC = PC[31-28] \parallel (IR[25-0] \ll 2)$
Memory access or R-type completion	$\text{Reg}[IR[15-11]] = ALUOut$	Load: $MDR = \text{Memory}[ALUOut]$ or Store: $\text{Memory}[ALUOut] = B$		
Memory read completion		Load: $\text{Reg}[IR[20-16]] = MDR$		

# Summary

- In multicycle datapath it takes different number of clock cycles for different instructions.
- We need several registers to store intermediate results in multicycle datapath.
- We need only one memory and one ALU since they can be used for different purposes in different clock cycle.